

CAUTION

Lithium batteries can be extremely dangerous, if not handled and cared for properly. This design does not include any form of current limiting circuit, like a fuse. So, care must be taken to ensure that the wiring guidelines are followed accurately, that checks are made for short-circuits, and that battery polarities are marked, and they are inserted the correct way round. Failure to do so, could result in an explosive fire.



Charging Practices: Always remove batteries from your project to charge them. Use a charger, designed for the battery used, and from a trusted supplier. Choose a flat, non-flammable surface to charge on, away from flammable materials. Never leave unattended when charging. Don't charge overnight. Monitor charging to ensure charge characteristics are as expected. Only pair batteries with similar characteristics. Do not overcharge, or leave charging for prolonged periods. This increases the risk of damage and fire.



Battery care & maintenance: Stop using a battery if it is swollen, damaged, dented or leaking. Never charge a damaged battery. Never allow a Lithium battery to discharge below 3.2 volts, as cell damage will occur. Avoid extreme temperatures. Do not charge or store batteries in very hot or cold environments. Don't cover batteries whilst charging, as this can trap heat, causing overheating.

In case of fire: Get out and stay out. If a fire starts, leave immediately, and call the fire brigade. For low voltage Lithium batteries, water is a safe extinguisher.

Built-in Monitoring: Most of my project designs include code, and circuitry, to monitor battery voltage, whilst in use. This code then seeks to alert the operator, when the battery has reached a critical low voltage, before shutting down power consuming circuitry; including the micro. Time should therefore be spent on calibrating this feature, as a precaution, for good battery management and maintenance.

Carefully dispose of batteries that damaged, or discharged below their critical voltage.



Hand Tools:


Fine Nosed Pliers
Side Cutters
M3 Tap
M4 Tap
1.5 mm Drill
2.0 mm Drill
Needle Files
Screwdriver
Craft Knife



Note: Not all items
are shown here.

Tools & Materials:

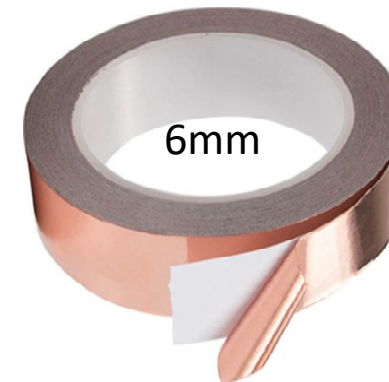- Temperature controlled iron
- Solder flux
- Resin cored solder
- 6mm adhesive copper tape
- Screw drivers
- Wire wrapping tool
- Wire wrapping wire 30 AWG





PCA9685 power lines

It is recommended that the GND and V+ lines on the PCA9685 are strengthened using insulated wire if significant currents are to be drawn from this pcb. This modification needs to be done in advance of assembling your robot.


The assignment of servos to PWM channels has been done symmetrically in such a way as to ease the cable runs to the servos in each leg. See a later slide that details this.

Only 11 of the 16 available channels have been used in this project, leaving scope for additional servos, used in arms, etc.

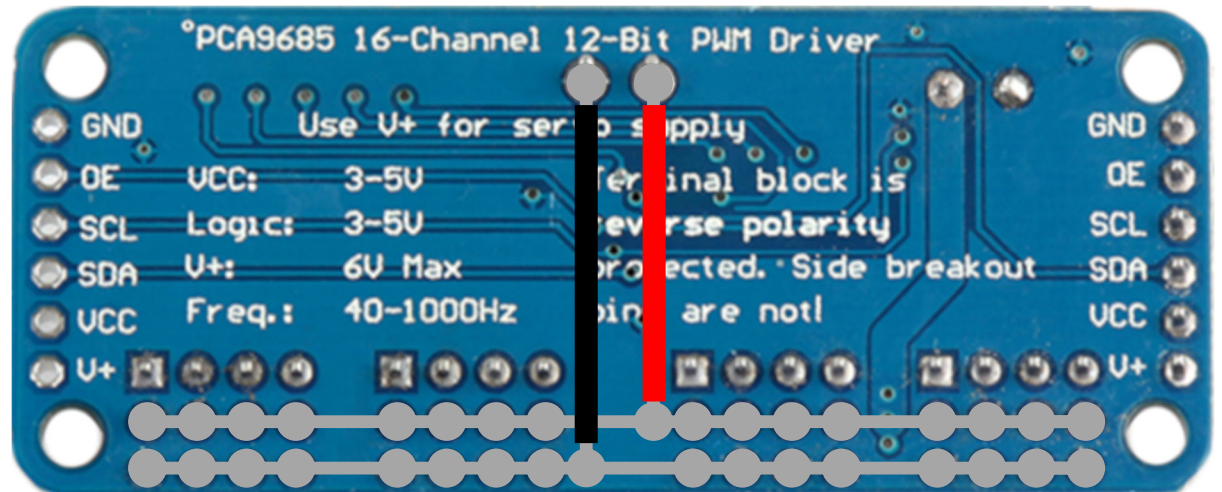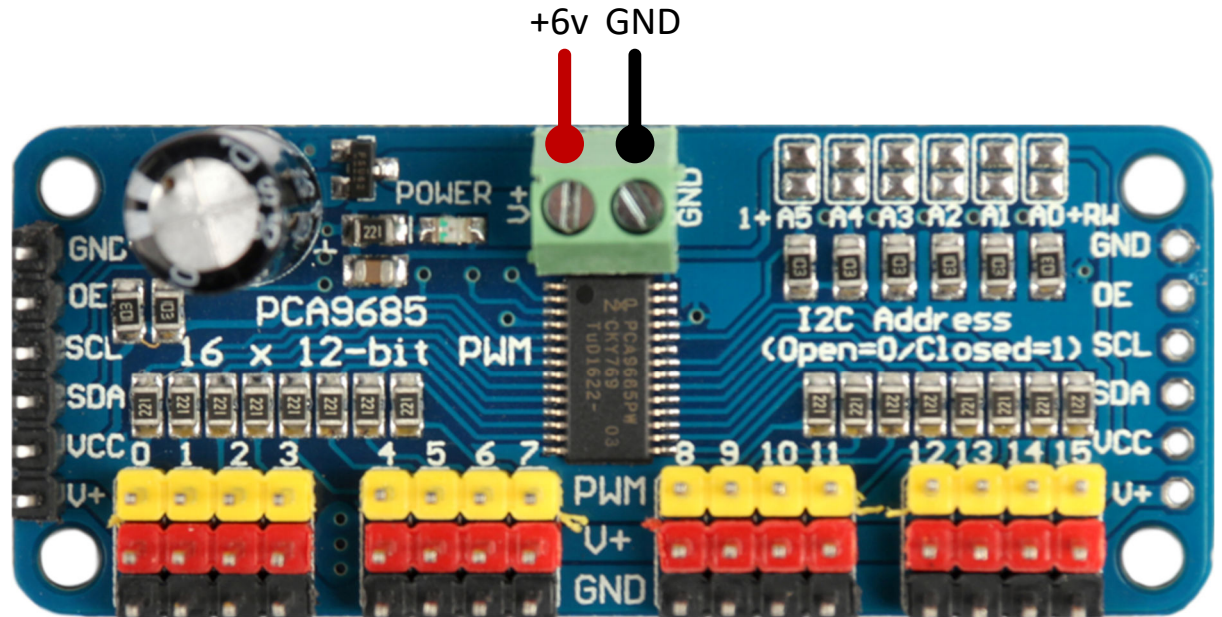The interface to the board is serial I2C bus. If more than 16 channels are needed then more PCA9685 boards can be connected in series, by simply extending the I2C bus and changing the default address of each board that is added.





Biped Droid Body Plate Wiring

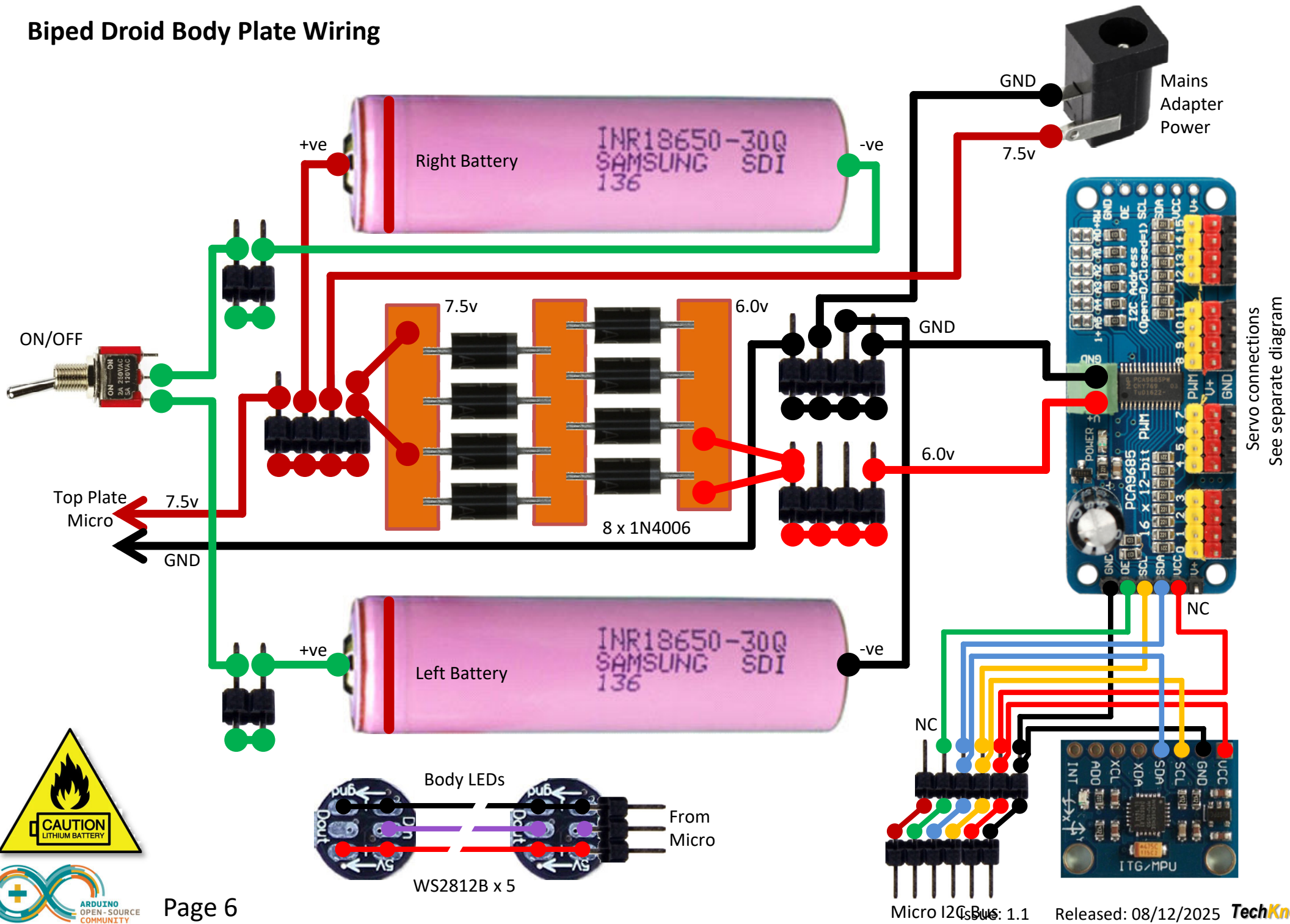


Servo connections
See separate diagram




Biped Droid Body Plate Wiring

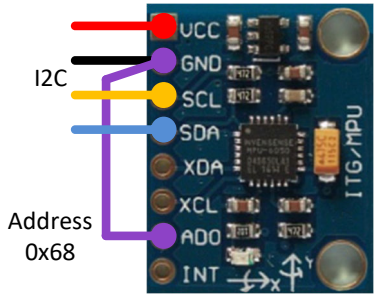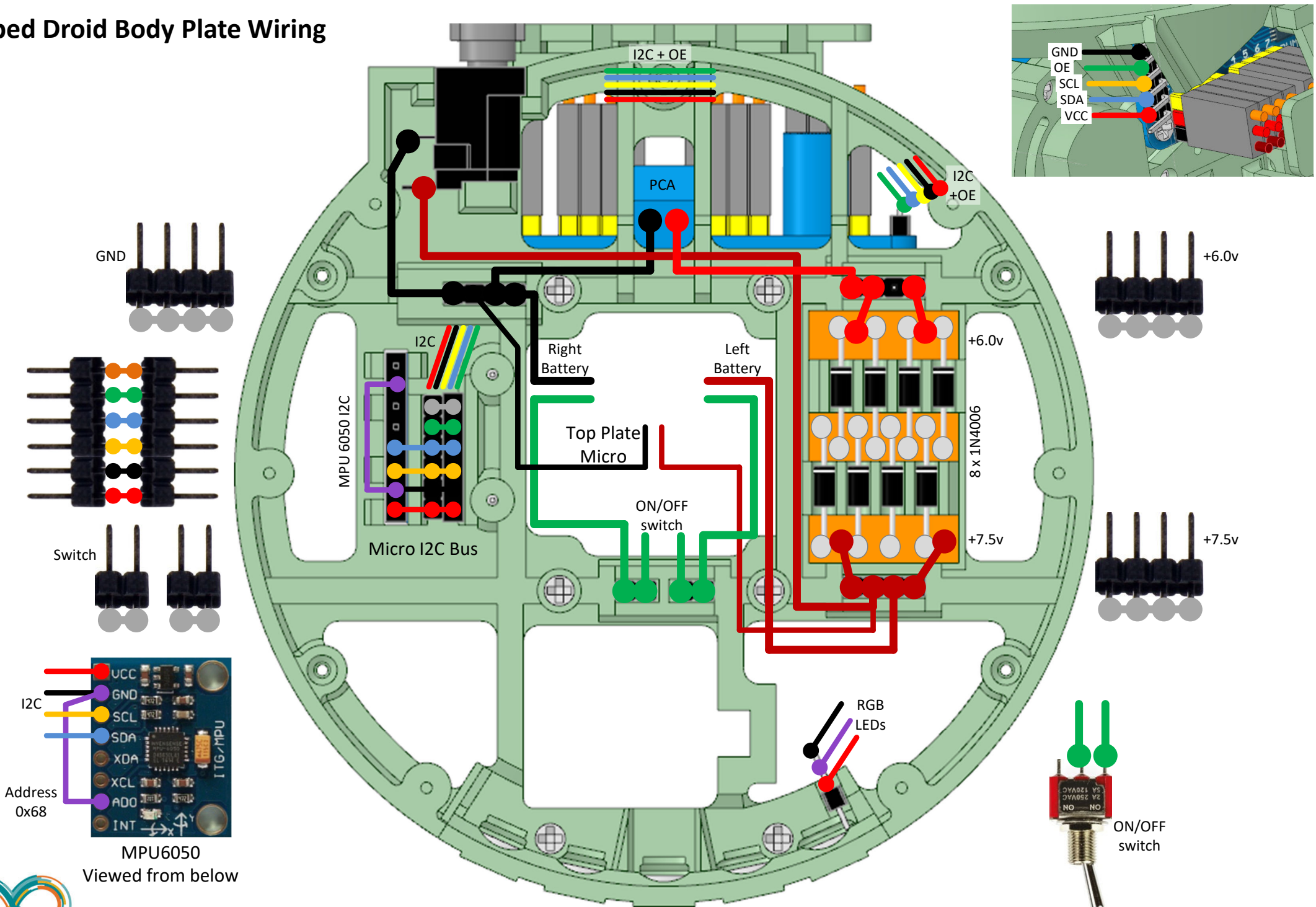


MPU6050
Viewed from below

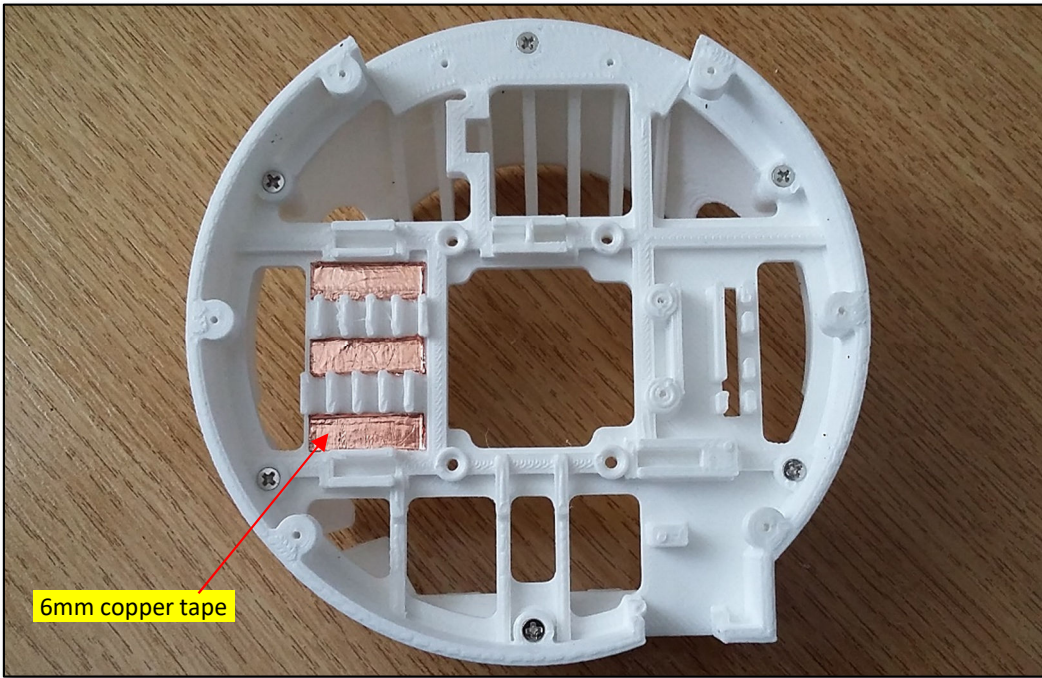


6mm copper tape

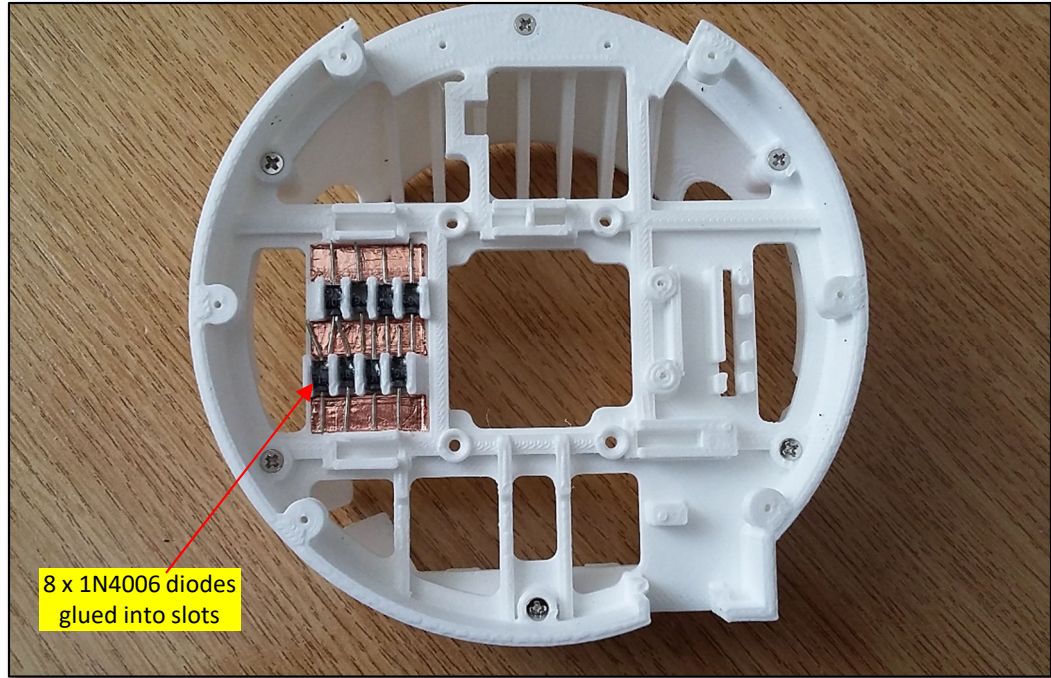

8 x 1N4006 diodes
glued into slots

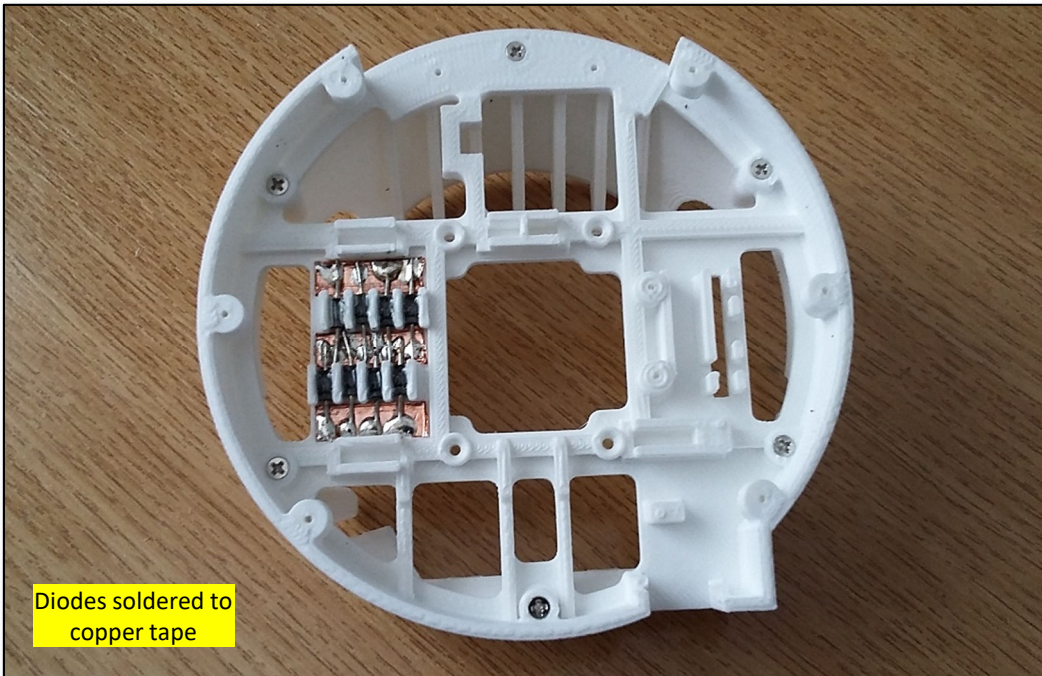


Diodes soldered to
copper tape

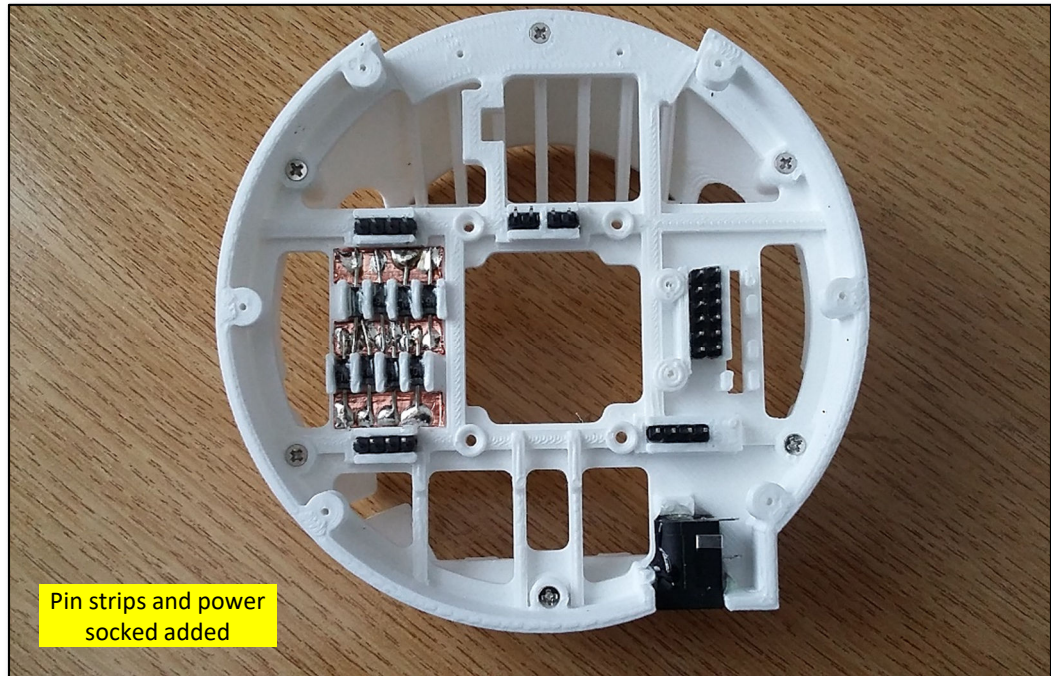

Pin strips and power
socket added


Servo Wiring

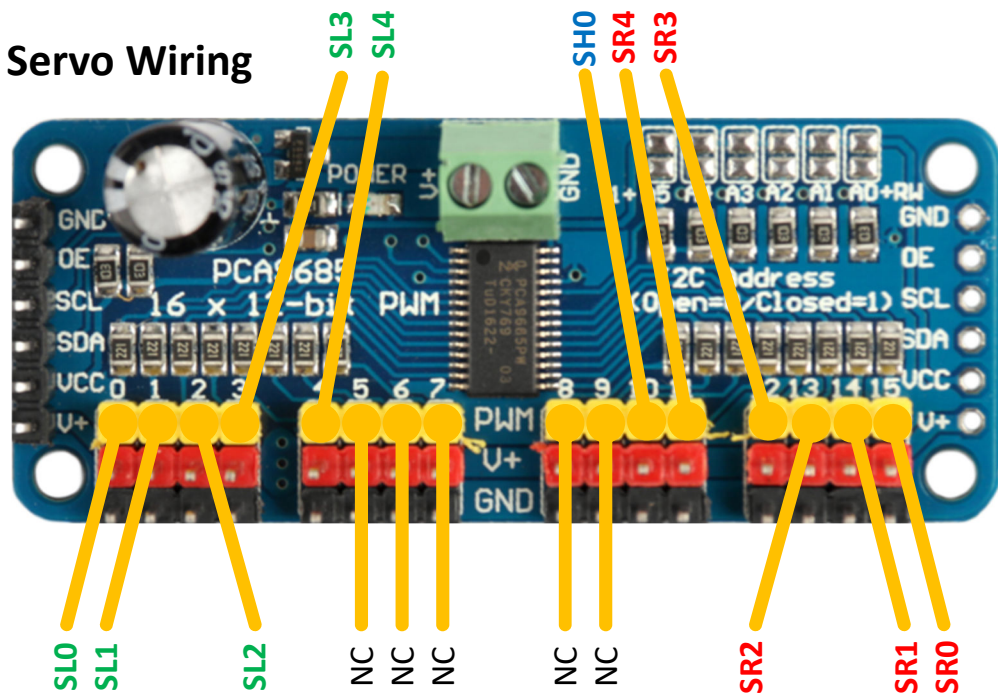


Wiring order:

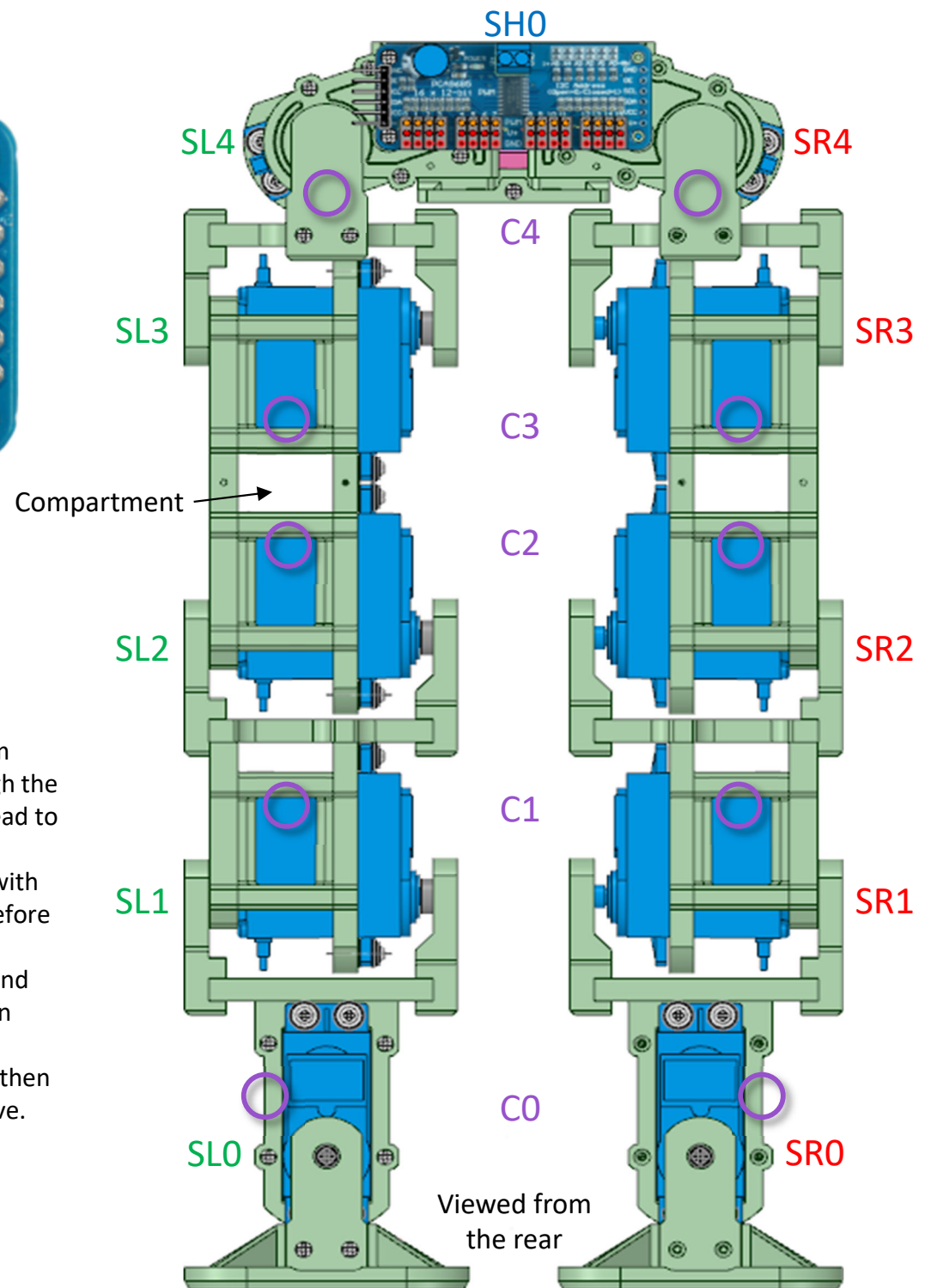1. Fit the front compartment covers.
2. Place the robot face down on a flat surface.
3. Pass SL0 lead through the 3 clips (C0,C1,C2) before attaching the 100mm extension cable. Then pass that lead through clip C4. Then pass SL1 through the 4 clips (C1,C2,C3,C4). Manipulate the left foot and knee joint to pull SL0 lead to its maximum extension. Now tie SL0 to SL1 between clips C1 and C2.
4. Pass SL2 leader through the 3 top clips (C2,C3,C4). Bend the knee joint with the foot as far forward as possible to pull on the leads, then tension SL2 before applying cable ties.
5. Bring the SL3 lead down through clip C3, loop it into the compartment and then back through clips C3 and C4. The compartment acts as a space within which spare cable length can be gathered and hidden from view.
6. Lead SL4 will pass over the servo and under the body to the top centre, then out through the back of the body to connect to the driver board from above.
7. Repeat these steps for the right-hand side servos SR0 to SR4.

Also view the photo on the following slide




Servo Wiring

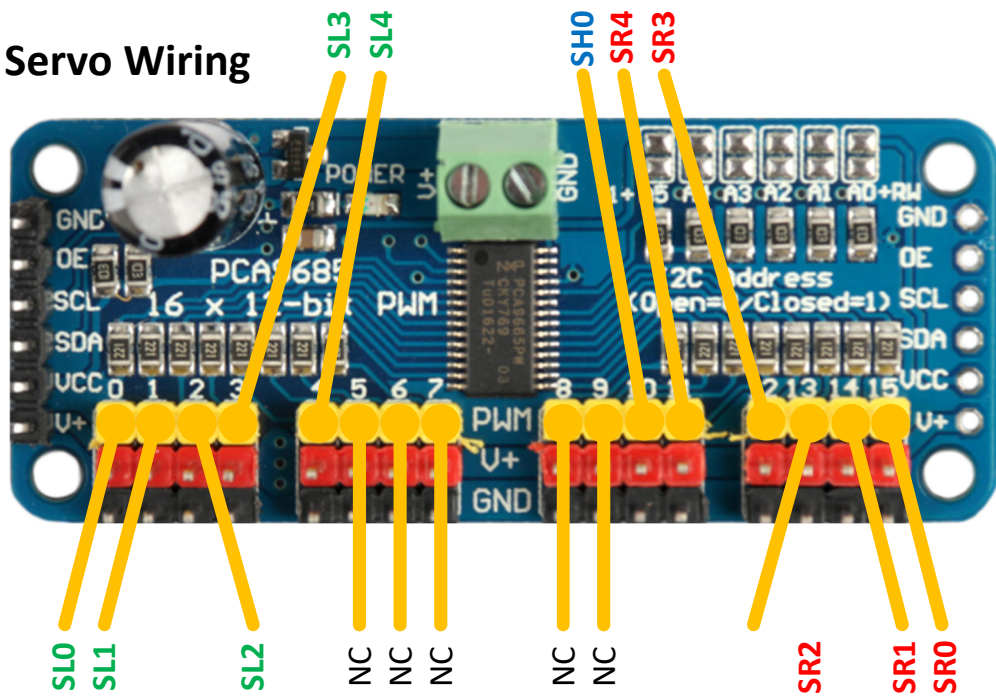


Wiring order repeated:

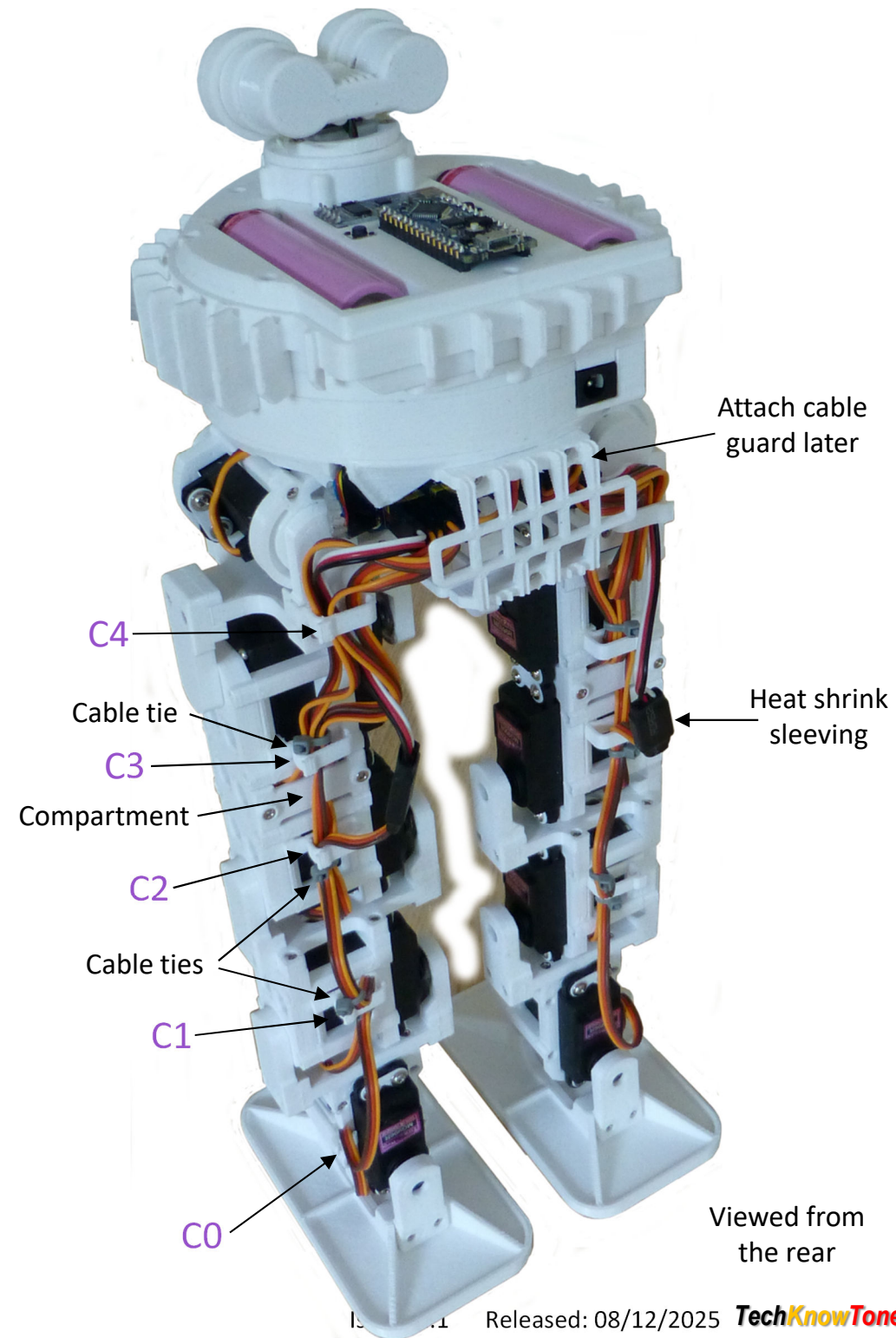1. Place the robot face down on a flat surface.
2. Pass SL0 lead through the 3 clips (C0,C1,C2) before attaching the 100mm extension cable. Then pass that lead through clip C4. Then pass SL1 through the 4 clips (C1,C2,C3,C4). Manipulate the left foot and knee joint to pull SL0 lead to its maximum extension. Now tie SL0 to SL1 between clips C1 and C2.
3. Pass SL2 leader through the 3 top clips (C2,C3,C4). Bend the knee joint with the foot as far forward as possible to pull on the leads, then tension SL2 before applying cable ties.
4. Bring the SL3 lead down through clip C3, loop it into the compartment and then back through clips C3 and C4. The compartment acts as a space within which spare cable length can be gathered and hidden from view.
5. Lead SL4 will pass over the servo and under the body to the top centre, then out through the back of the body to connect to the driver board from above.
6. Repeat these steps for the right-hand side servos SR0 to SR4.
7. Fit the rear compartment covers to hide the excess cables once you are happy with the slack in the cables, when the legs are bent over.




Biped Droid Top Plate Circuit


2.4GHz Wireless Transceiver

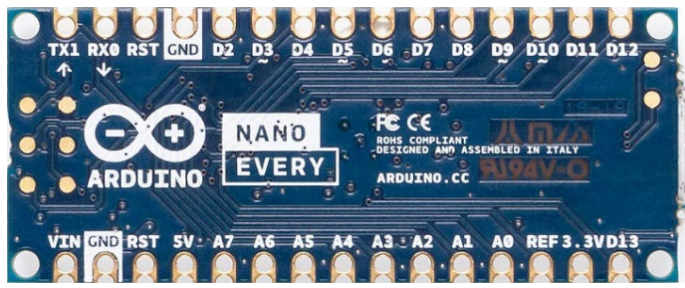



NANO EVERY underside view

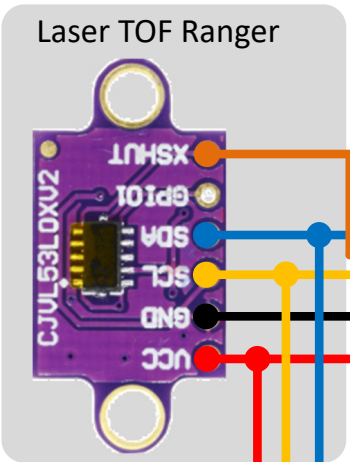


Laser TOF Ranger

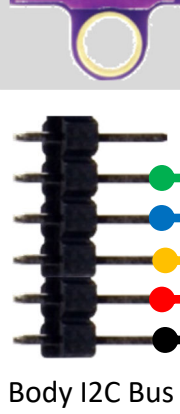

Body I2C Bus




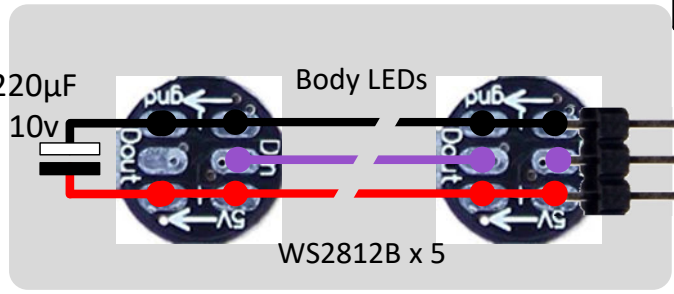
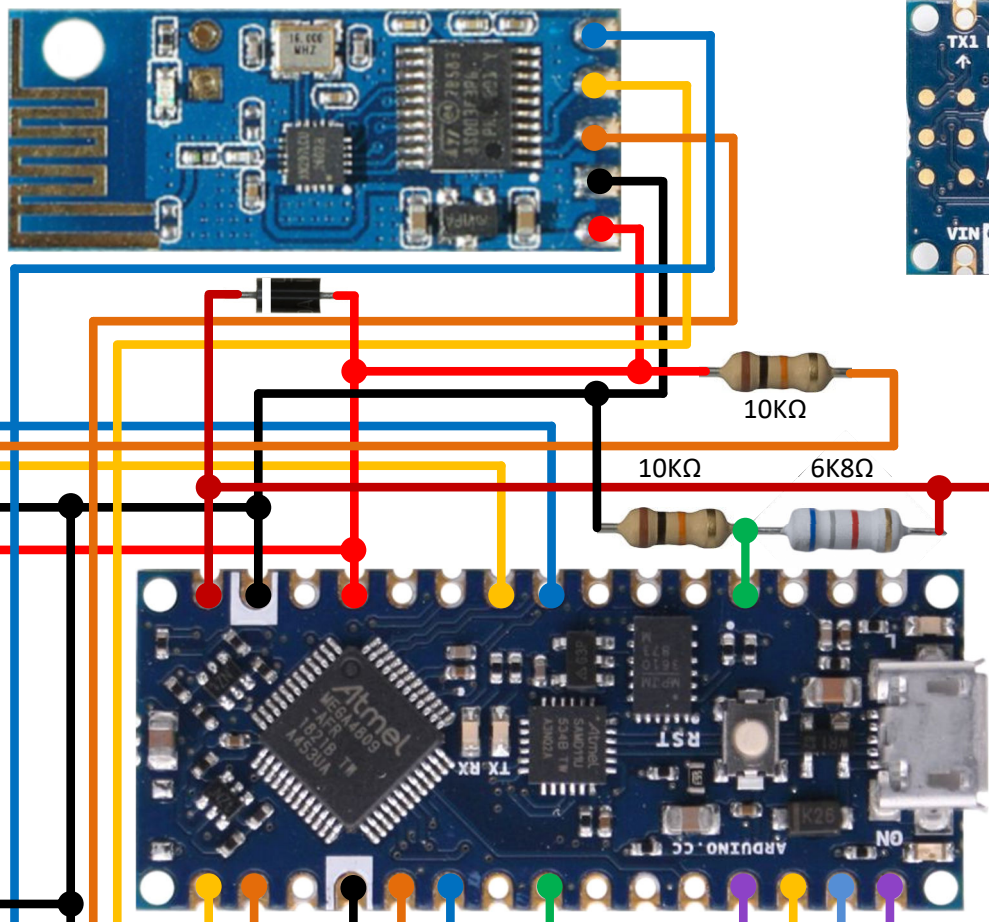






WS2812B x 5




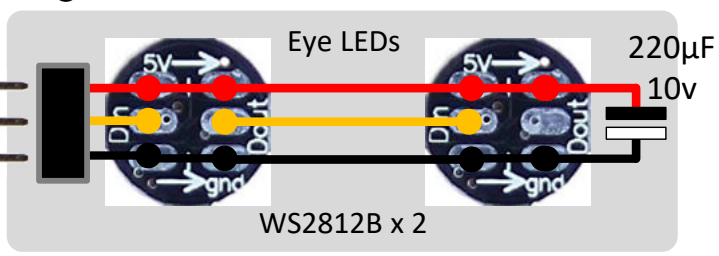



WS2812B x 2

Biped Droid Top Plate Wiring

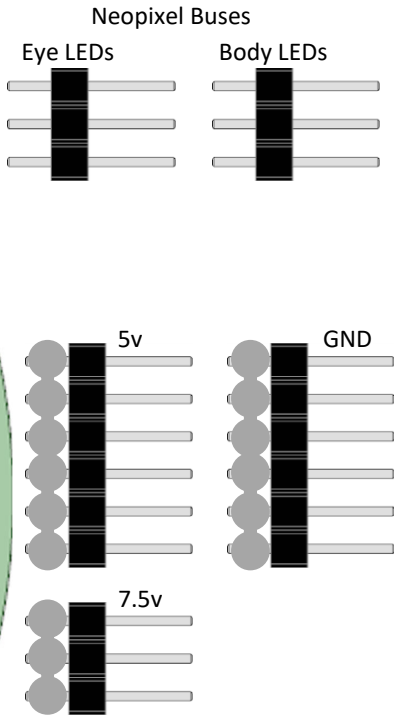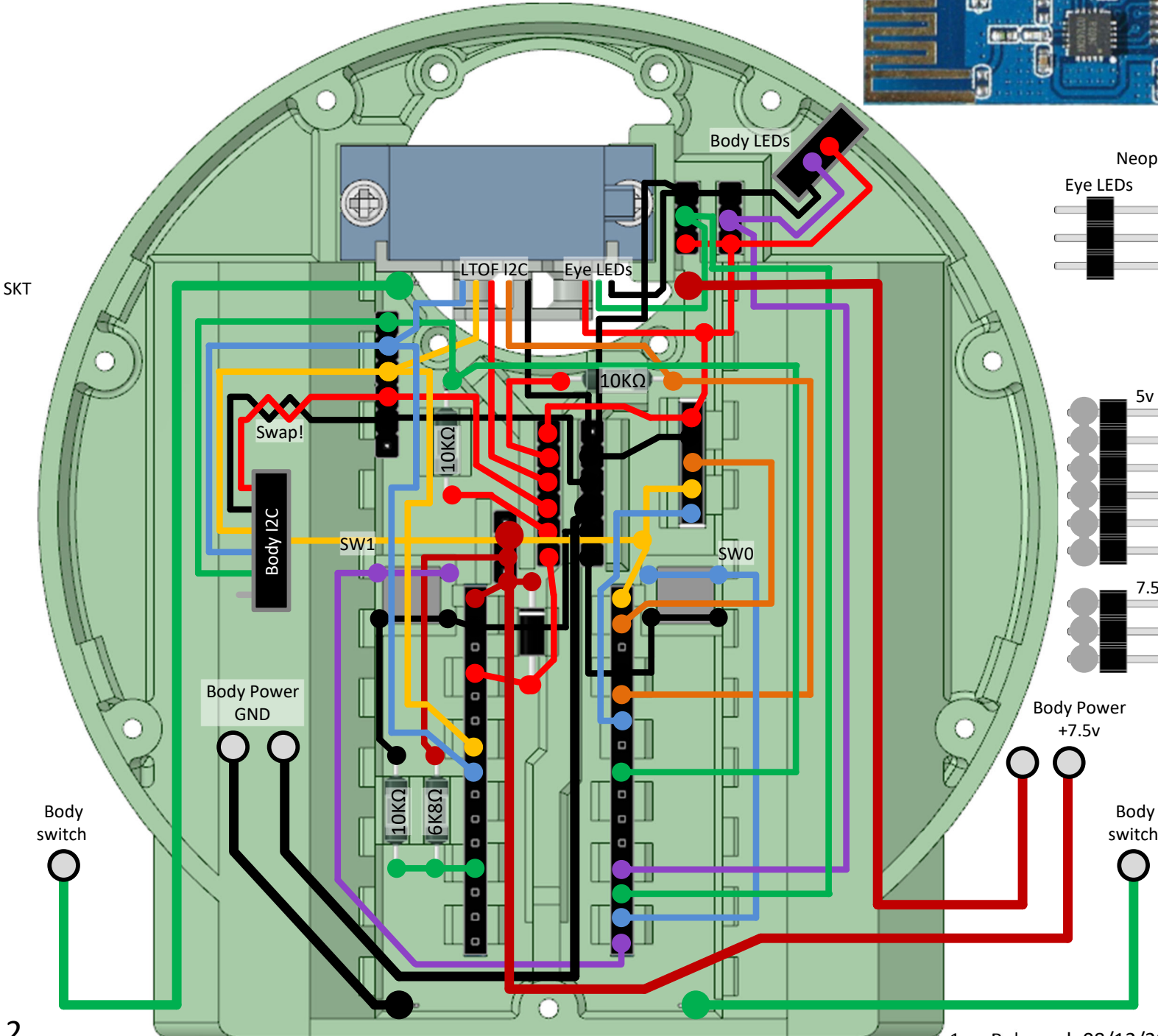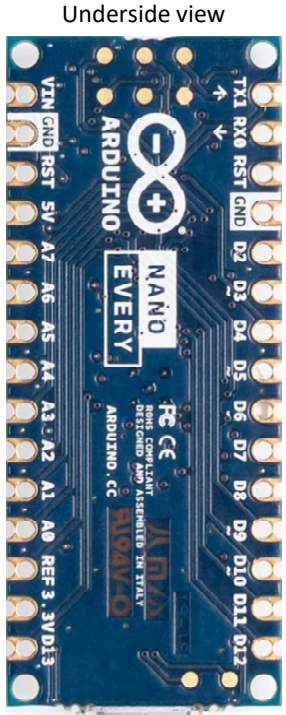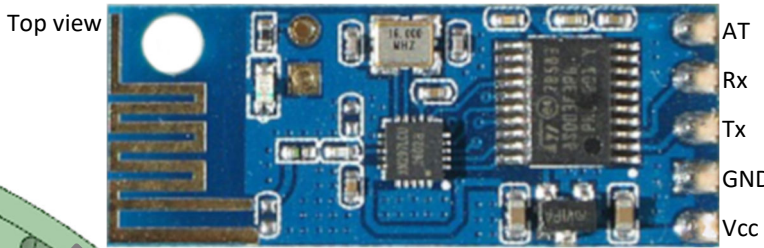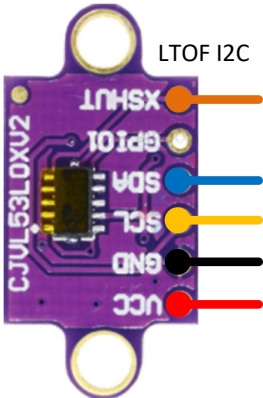


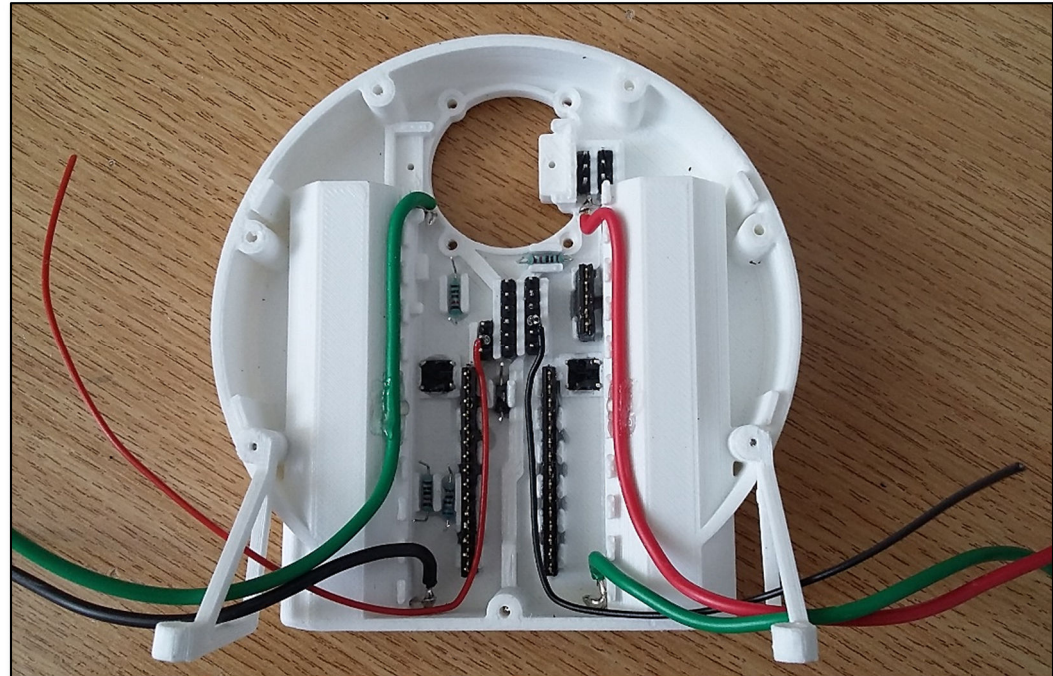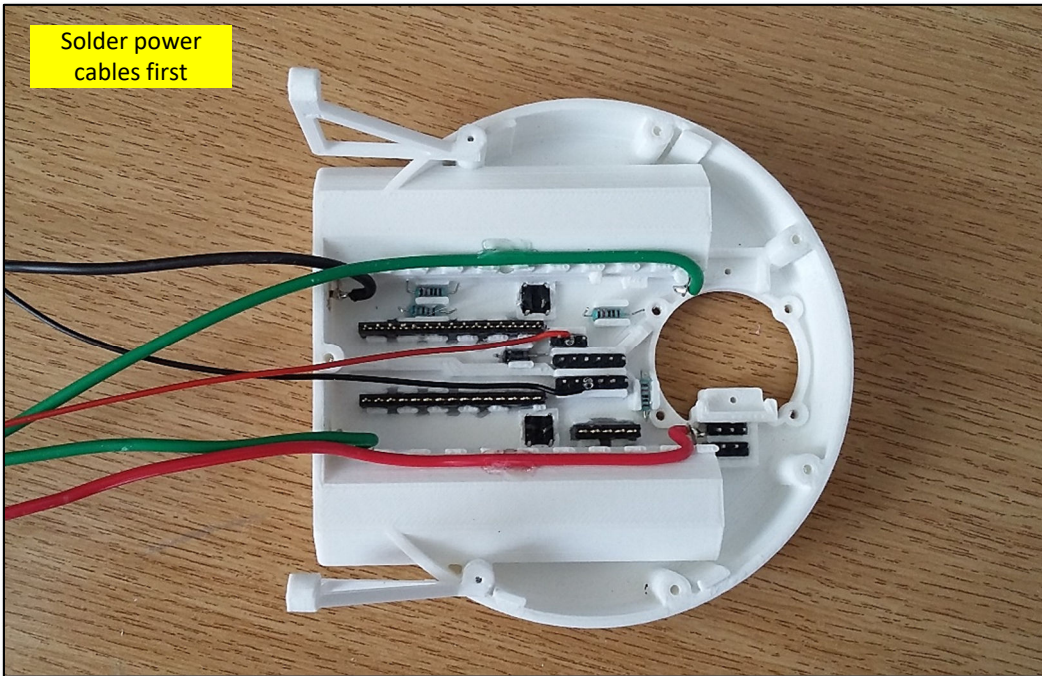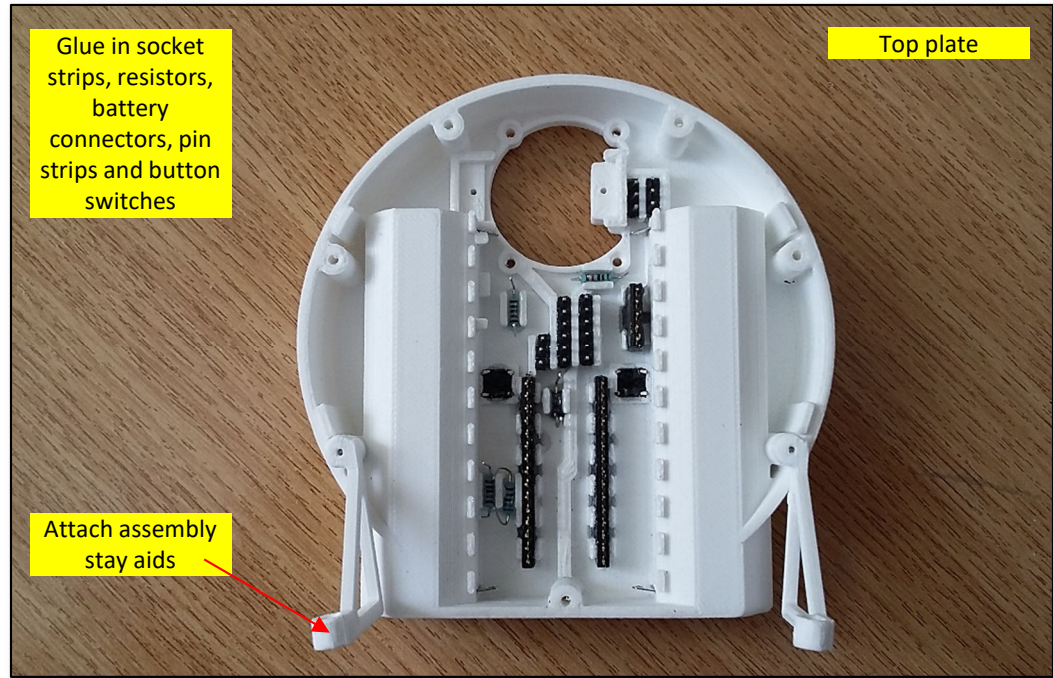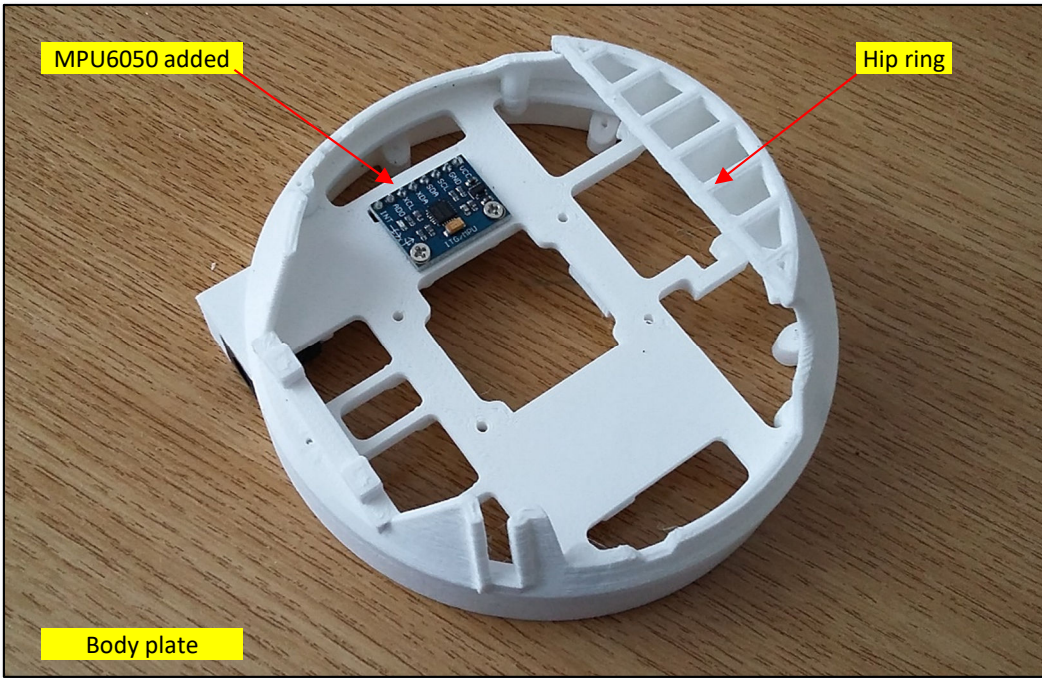

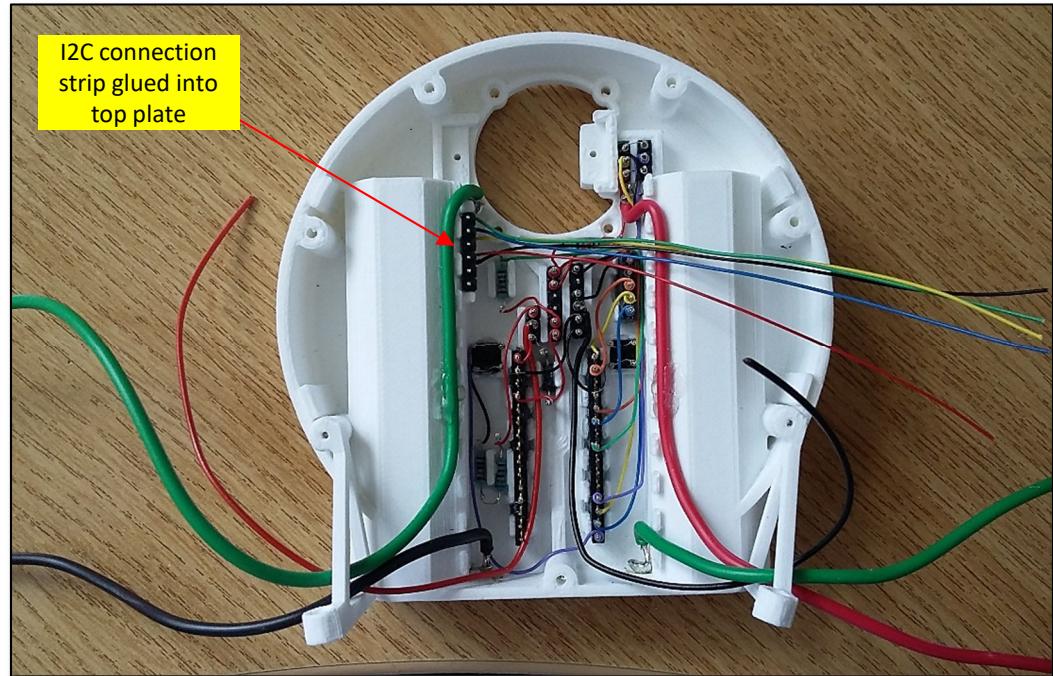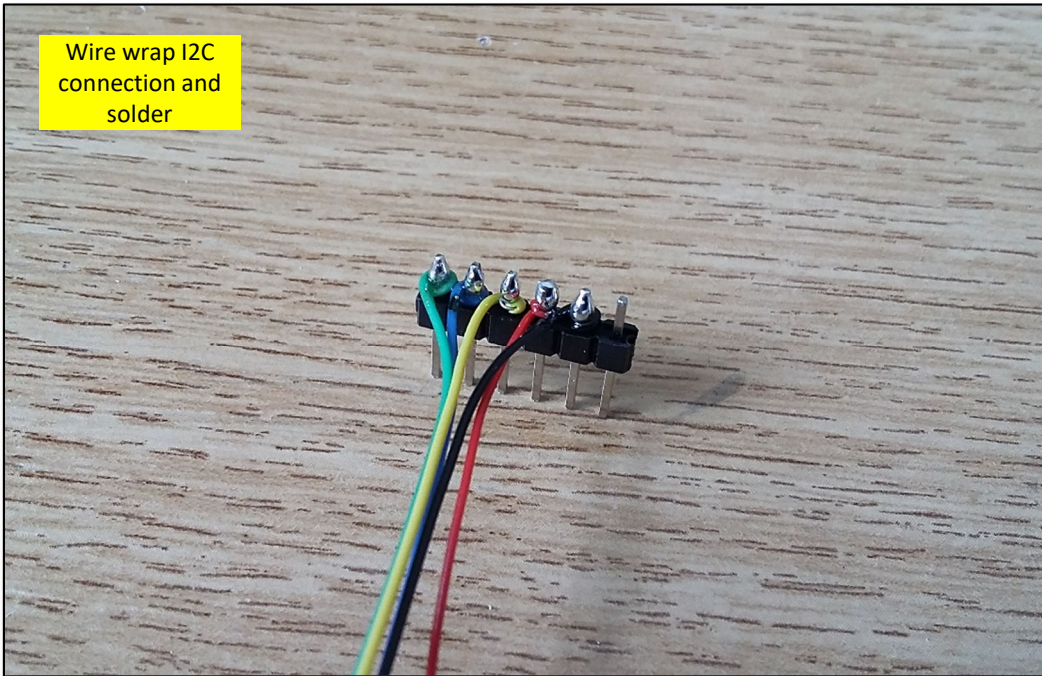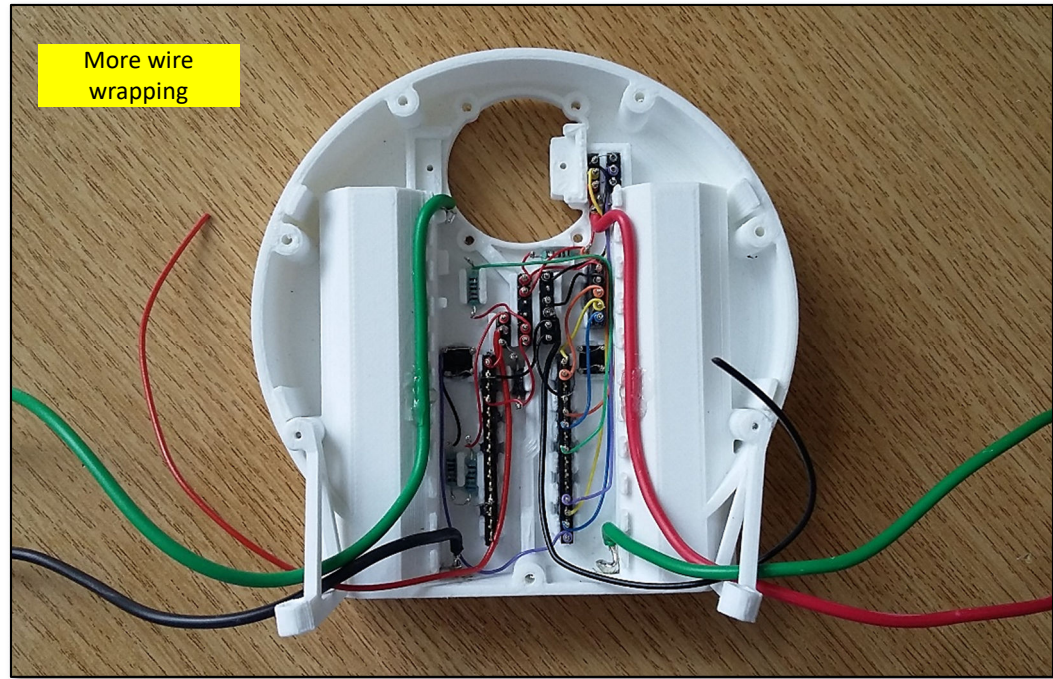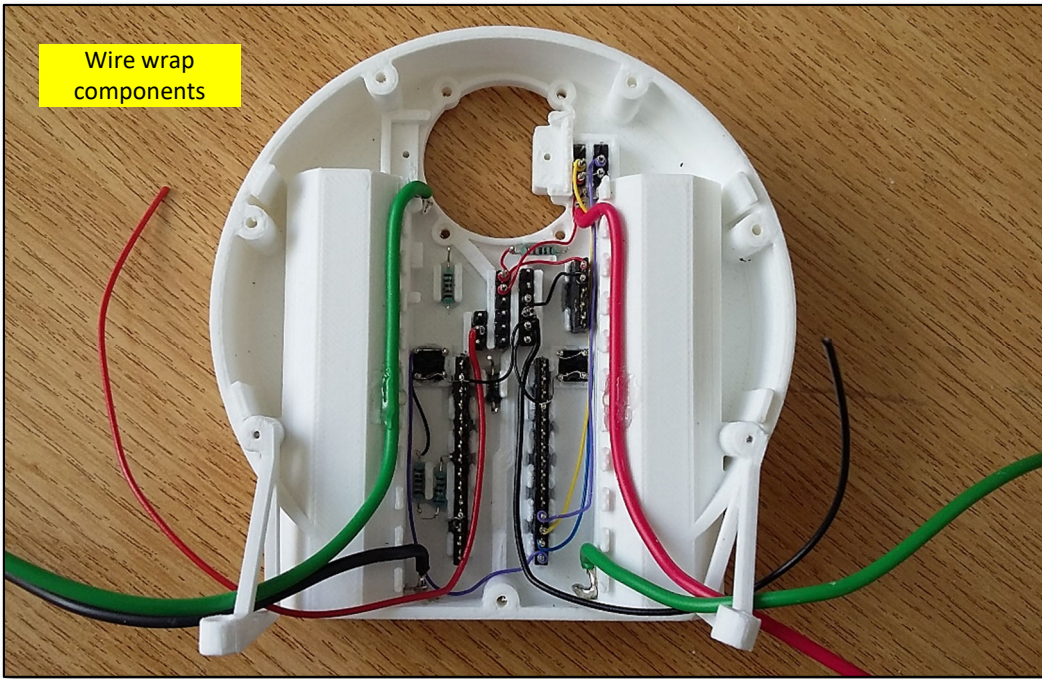

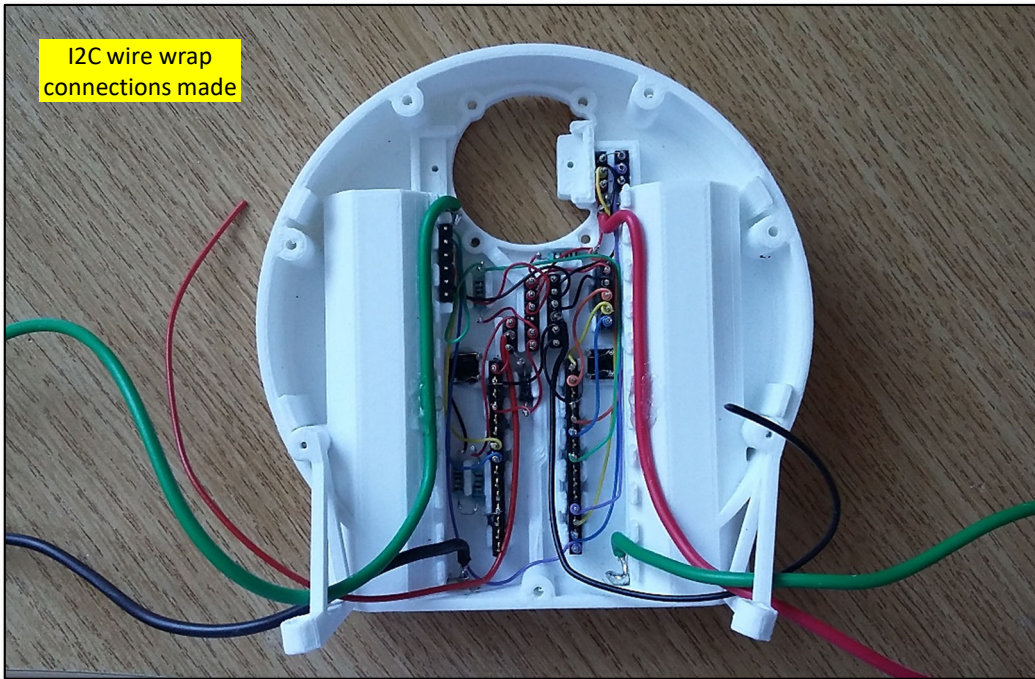

I2C wire wrap connections made

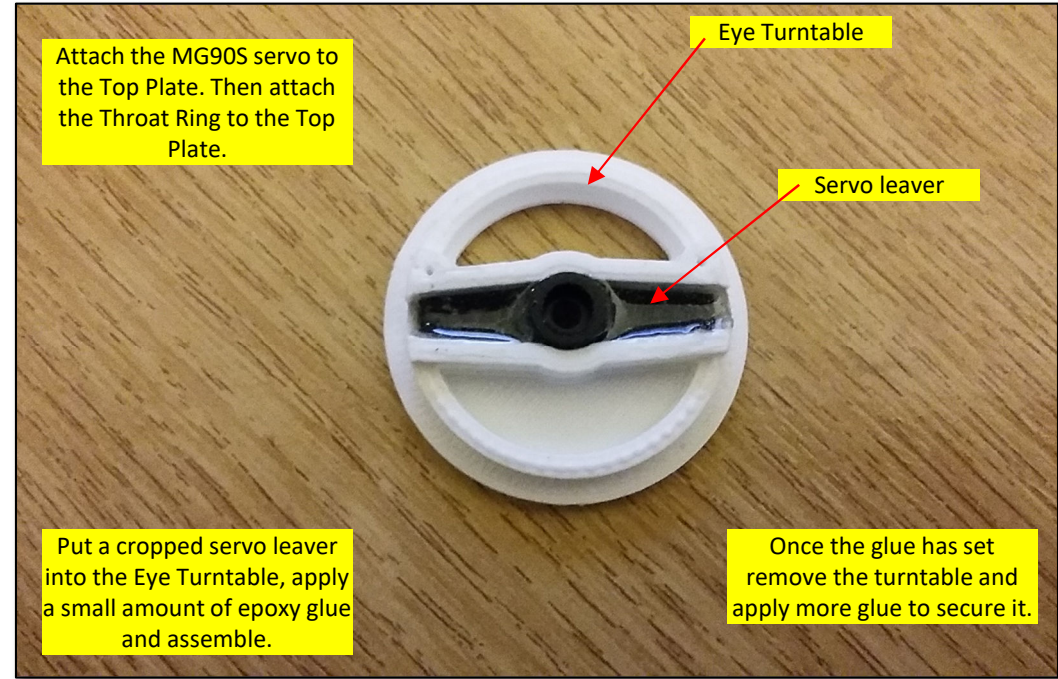


Attach the MG90S servo to the Top Plate. Then attach the Throat Ring to the Top Plate.

Eye Turntable


Servo lever

Put a cropped servo lever into the Eye Turntable, apply a small amount of epoxy glue and assemble.

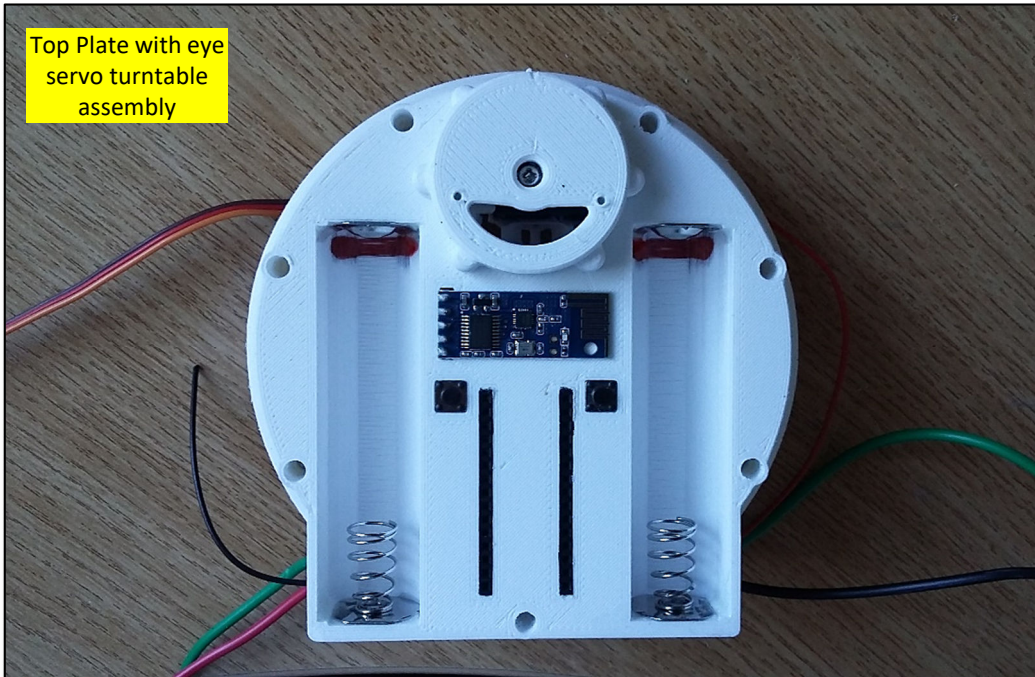Once the glue has set remove the turntable and apply more glue to secure it.







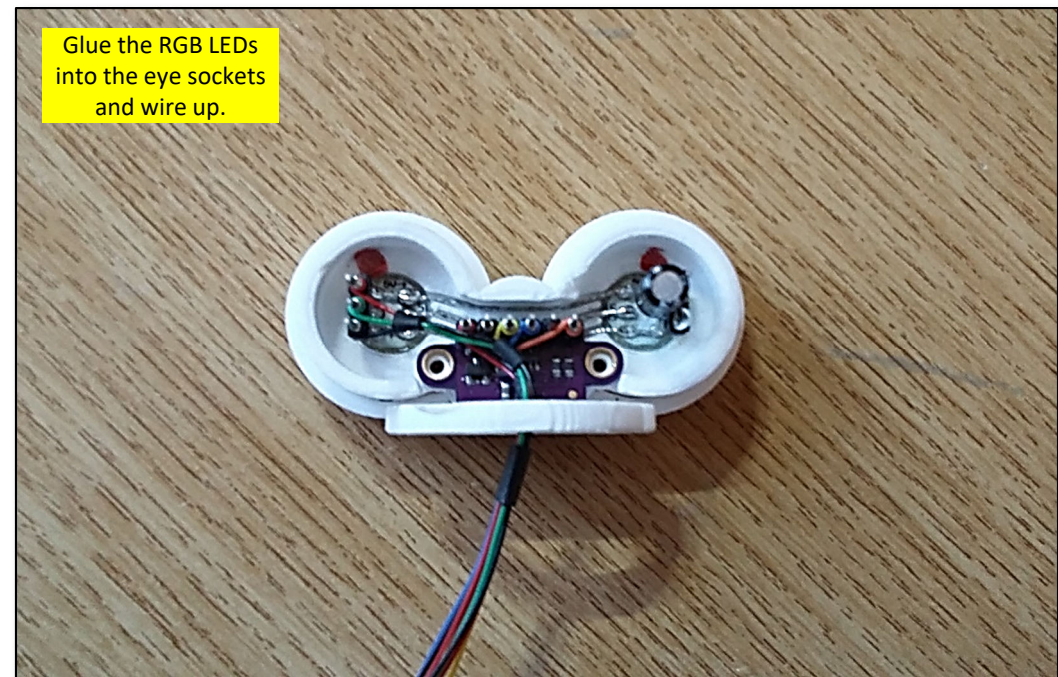
Top Plate with eye servo turntable assembly







Glue the RGB LEDs into the eye sockets and wire up.


Biped Droid Head Wiring

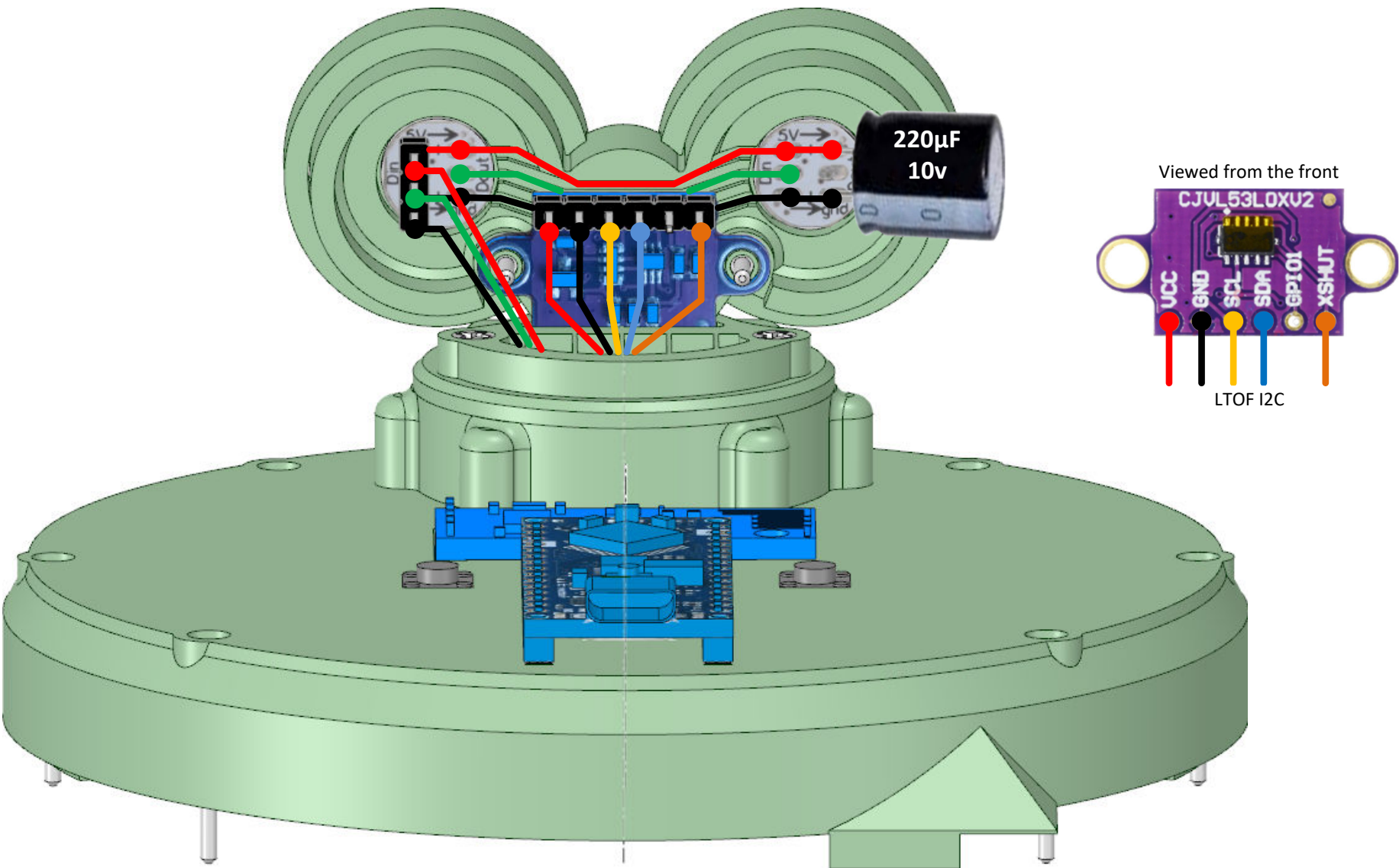

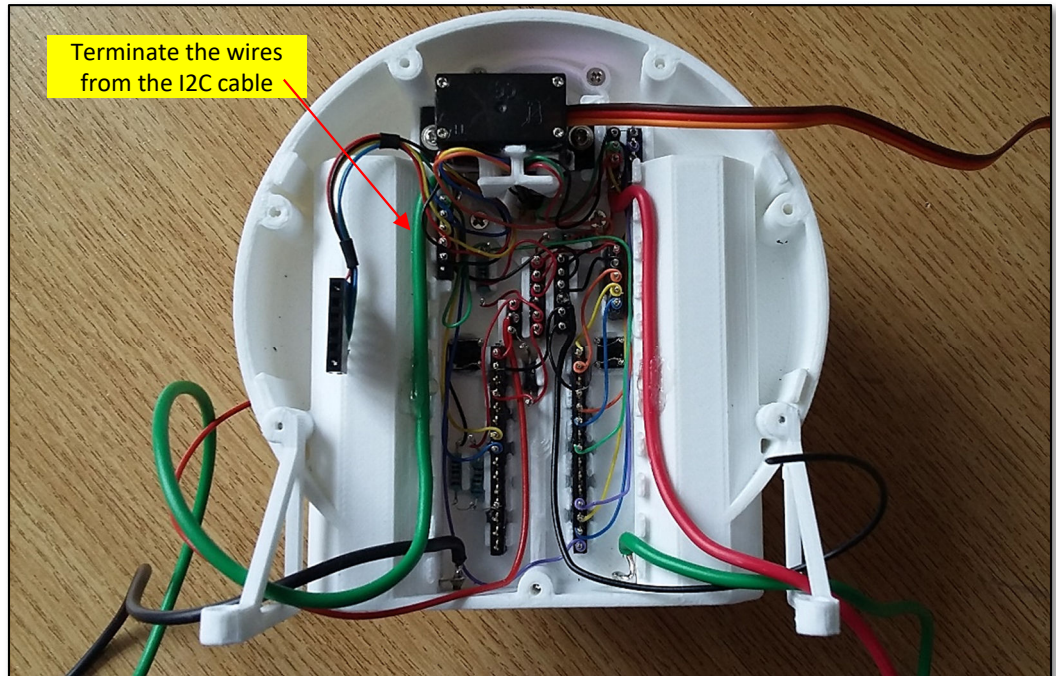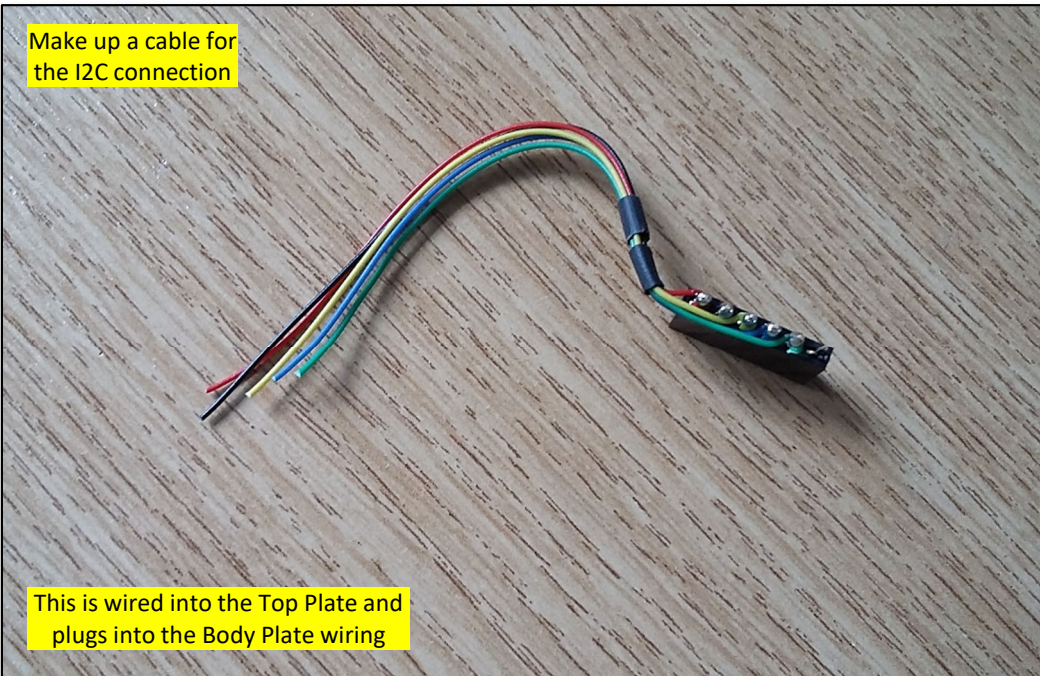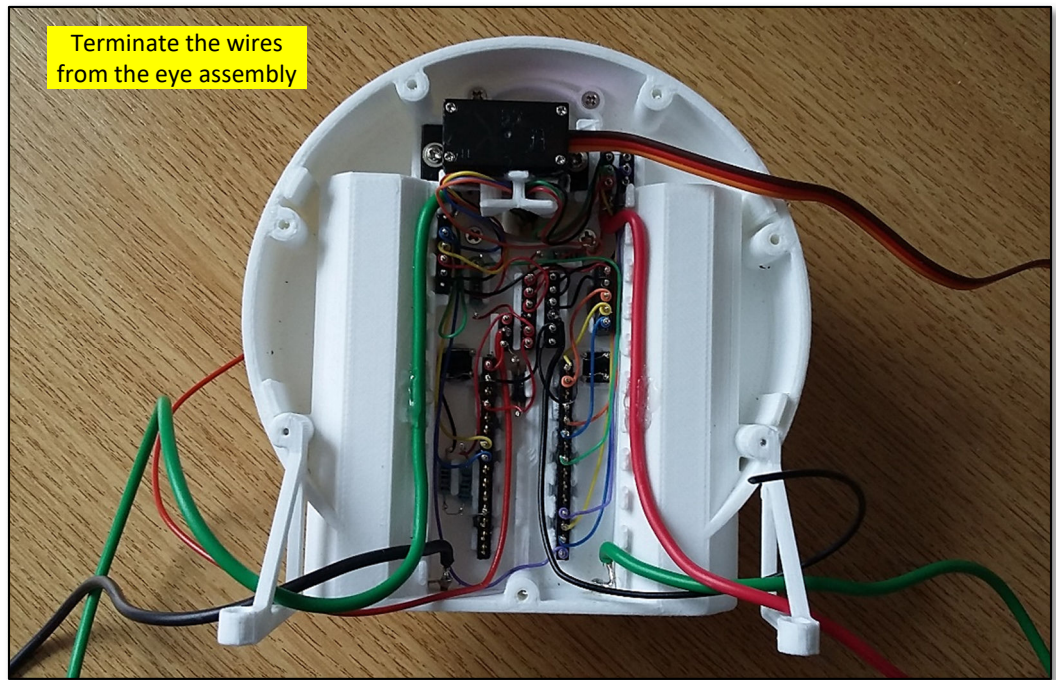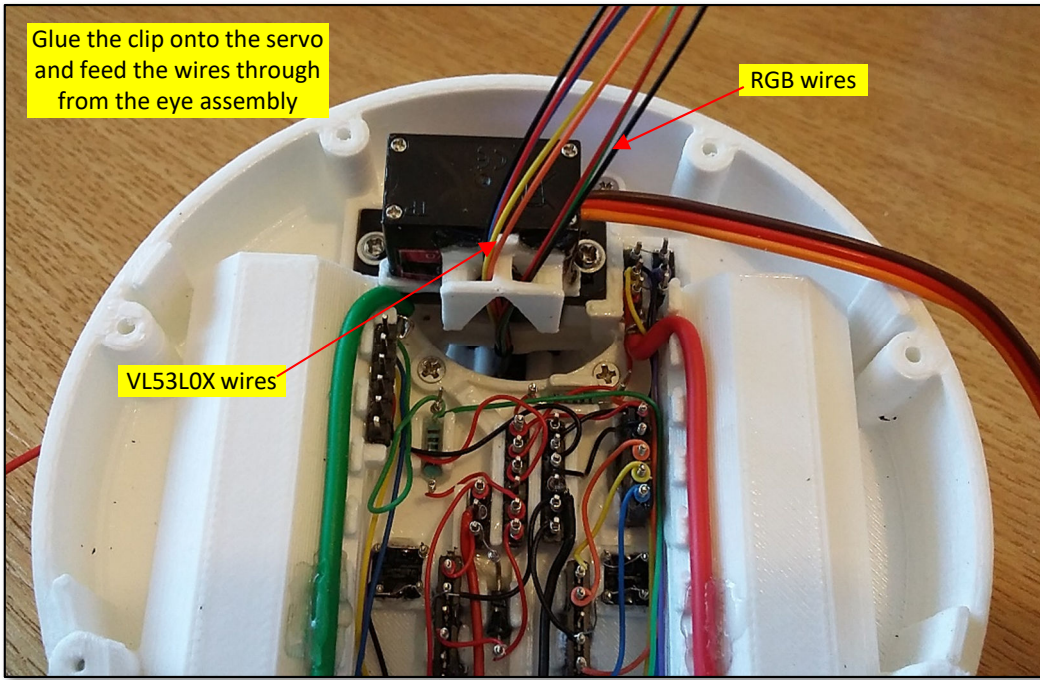

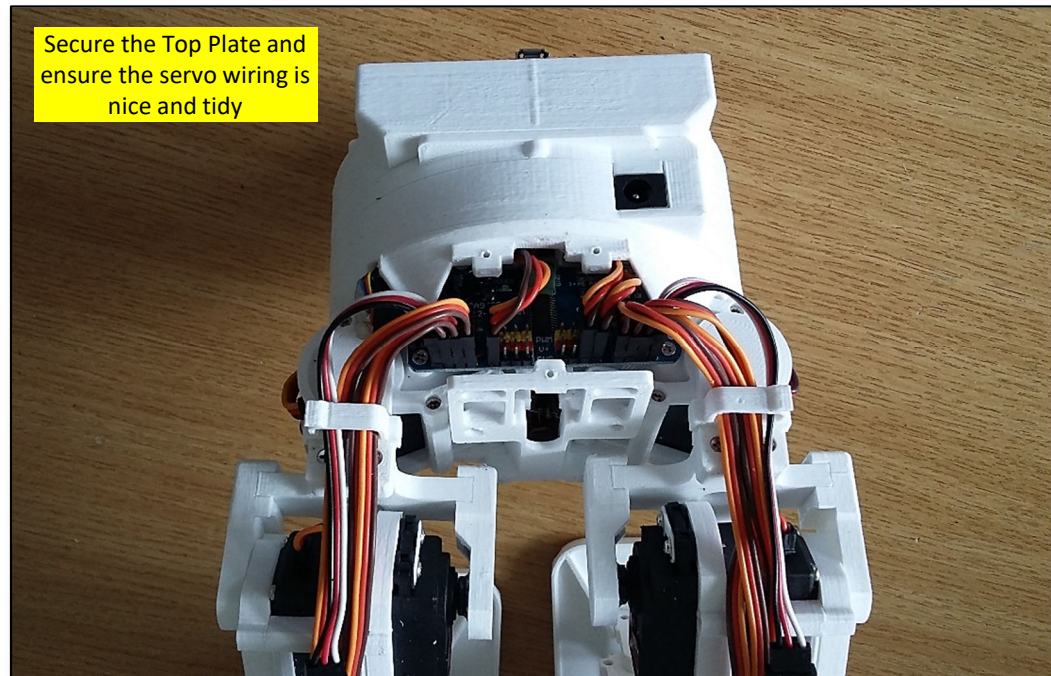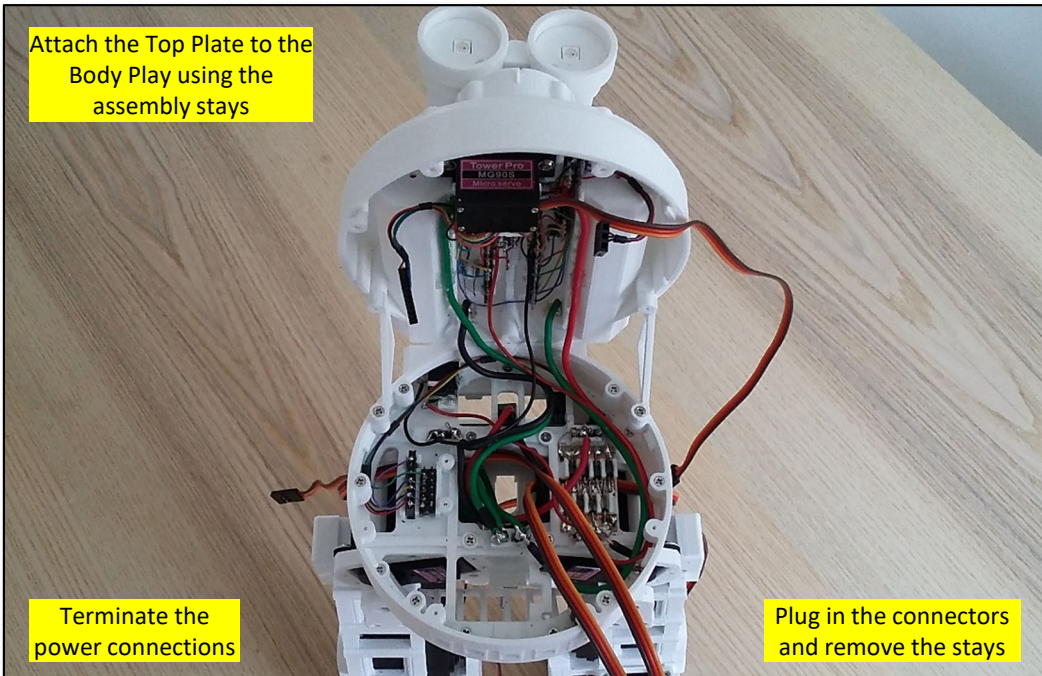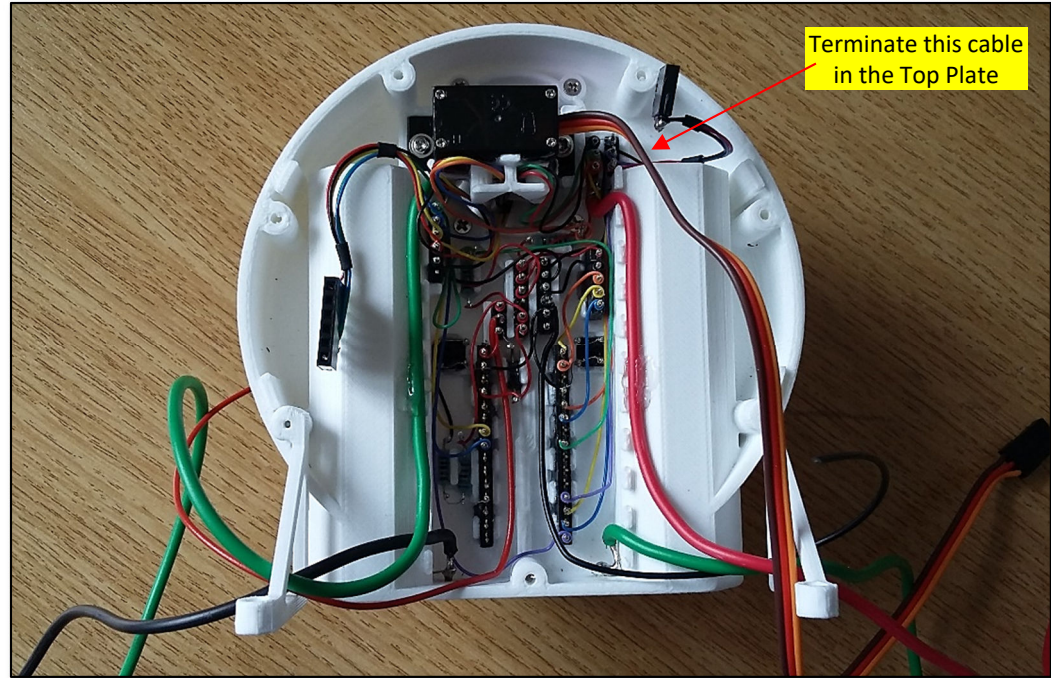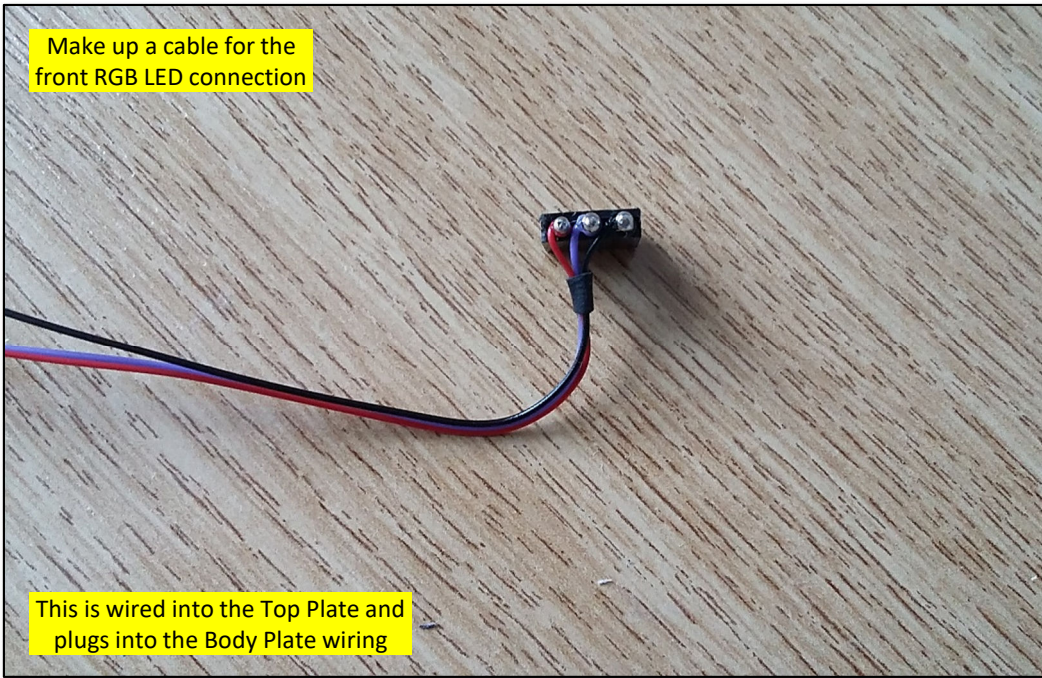

Battery Monitor (Protection)

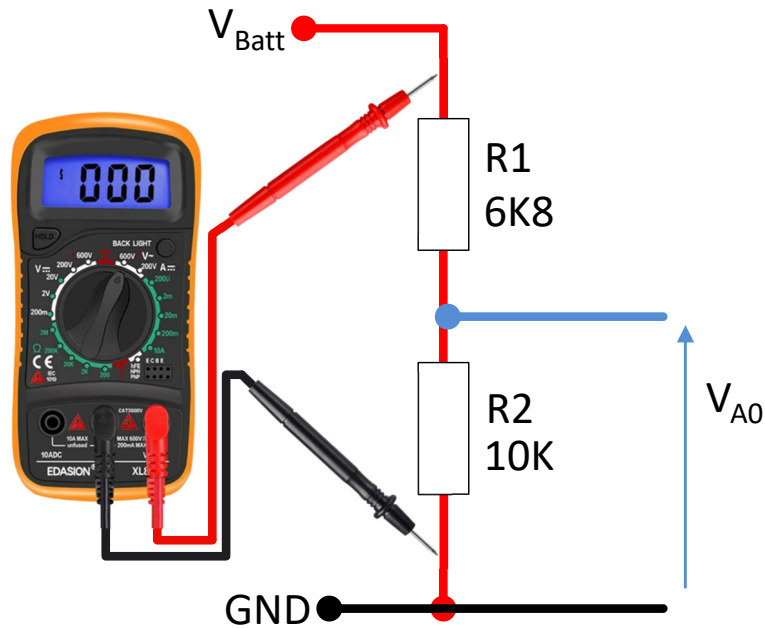

$$V_{A0} = \frac{V_{Batt} \times R2}{R1 + R2}$$

$$V_{A0D} = \frac{V_{A0} \times 1023}{5} \quad \text{voltage read by 10-bit ADC}$$

$$V_{A0} = \frac{V_{Batt} \times 10K}{16K8}$$

$$V_{A0D} = \frac{V_{Batt} \times 0.5952 \times 1023}{5}$$

$$V_{Batt} = \frac{V_{A0D} \times 5.0}{608.9}$$


$$V_{FSD} = 8.4v @ V_{A0} = 5v$$

Two cells in series gives a nominal 7.4v constant discharge voltage. To prevent damage, stop using once the following conditions are reached:

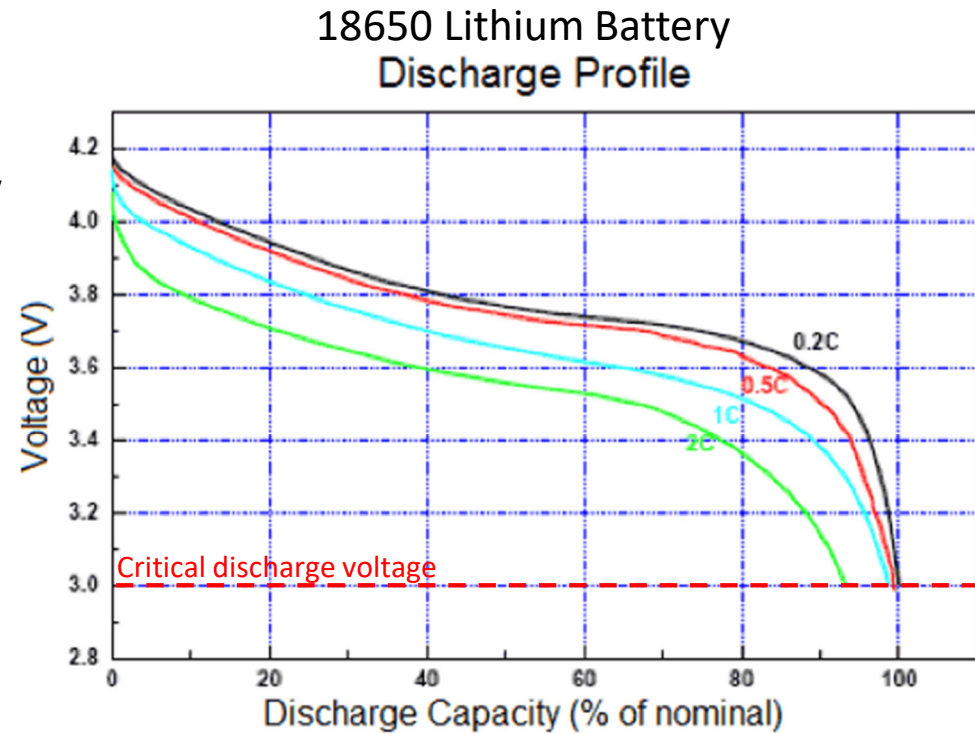- 3.60 + 3.00 = 6.60v (one battery fades early)
- 3.30 + 3.30 = 6.60v (both batteries fade together)

Hence $V_{A0D} = 540 @ V_{Batt} = 6.60v$

The code will shut down when the value drops to 540.



Discharge: 3.0V cutoff at room temperature.

