
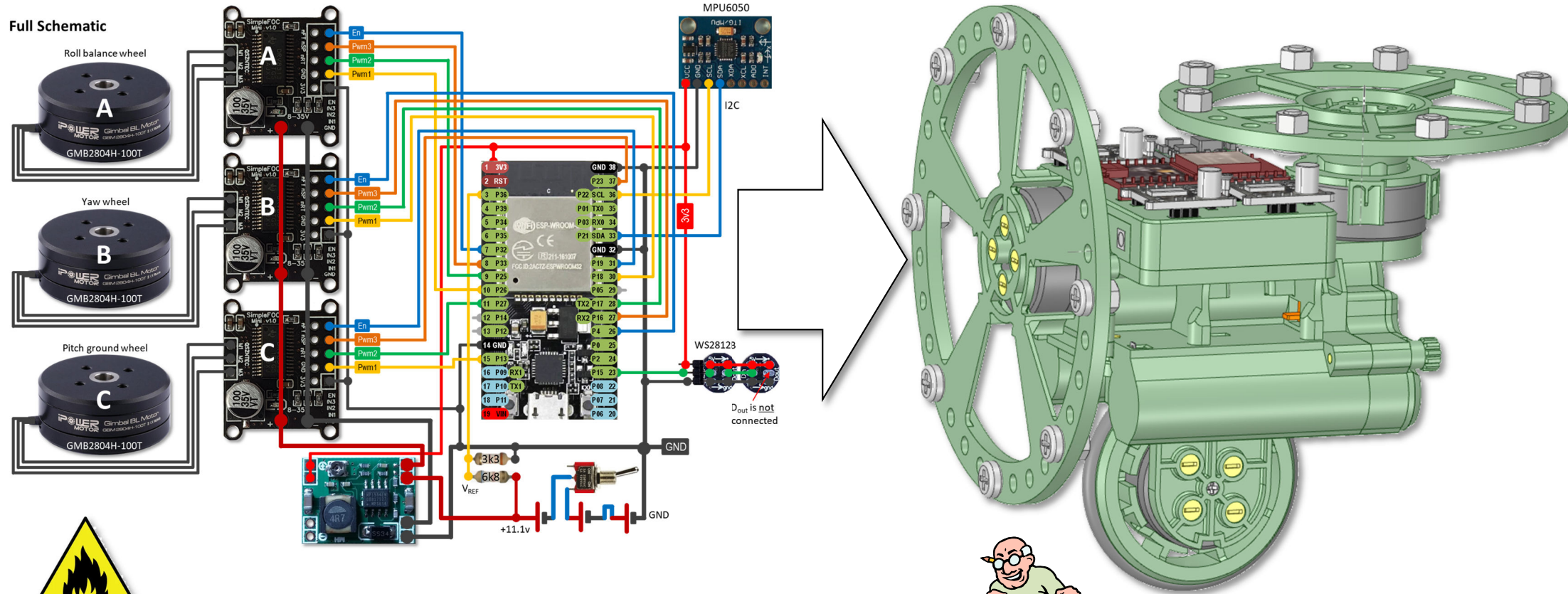


Uni-Bot (ESP32)

Circuits & Wiring

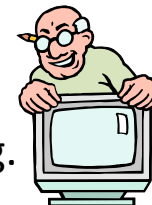

Read through the whole document before starting.



CAUTION

Lithium batteries can be extremely dangerous, if not handled and cared for properly. This design does not include any form of current limiting circuit, like a fuse. So, care must be taken to ensure that the wiring guidelines are followed accurately, that checks are made for short-circuits, and that battery polarities are marked, and they are inserted the correct way round. Failure to do so, could result in an explosive fire.



Charging Practices: Always remove batteries from your project to charge them. Use a charger, designed for the battery used, and from a trusted supplier. Choose a flat, non-flammable surface to charge on, away from flammable materials. Never leave unattended when charging. Don't charge overnight. Monitor charging to ensure charge characteristics are as expected. Only pair batteries with similar characteristics. Do not overcharge, or leave charging for prolonged periods. This increases the risk of damage and fire.



Battery care & maintenance: Stop using a battery if it is swollen, damaged, dented or leaking. Never charge a damaged battery. Never allow a Lithium battery to discharge below 3.2 volts, as cell damage will occur. Avoid extreme temperatures. Do not charge or store batteries in very hot or cold environments. Don't cover batteries whilst charging, as this can trap heat, causing overheating.

In case of fire: Get out and stay out. If a fire starts, leave immediately, and call the fire brigade. For low voltage Lithium batteries, water is a safe extinguisher.

Built-in Monitoring: Most of my project designs include code, and circuitry, to monitor battery voltage, whilst in use. This code then seeks to alert the operator, when the battery has reached a critical low voltage, before shutting down power consuming circuitry; including the micro. Time should therefore be spent on calibrating this feature, as a precaution, for good battery management and maintenance.

Carefully dispose of batteries that damaged, or discharged below their critical voltage.



Hand Tools:

Recommended:

- Fine Nosed Pliers
- Side Cutters
- 1.5 mm Drill
- 2.0 mm Drill
- 2.4 mm Drill
- 4.0 mm Drill
- M3 Tap
- Needle Files
- Screwdrivers
- Craft Knife



Note: Not all items needed are shown here.

Tools & Materials:

Temperature controlled iron

Solder flux

Resin cored solder

Hot melt glue gun {optional}

2-part epoxy resin glue

Screw drivers

Tweezers

Wire wrapping tool


Wire wrapping wire 30 AWG

24 AWG stranded wire (red, black & yellow)

Multimeter



Full Schematic

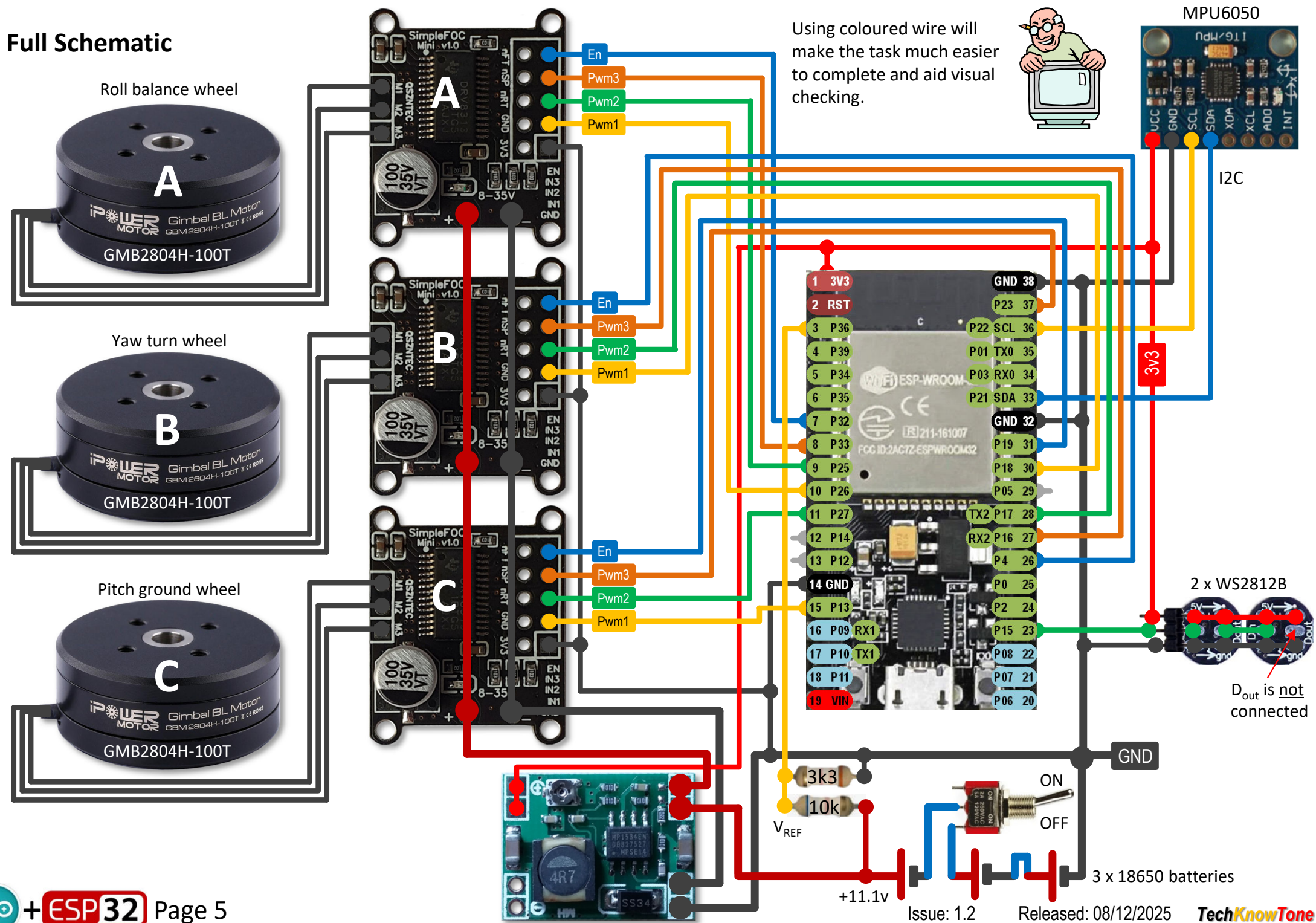

Micro Plate Wiring - Total





The micro plate hosts the majority of the wiring, with the device socket strips and pin strips acting as terminals, onto which the wires can be wrapped. Two small support brackets are used to hold the Micro Plate in a vertical position, next to the 'Turn' motor, to aid the wiring process.

The wires from the BLDC motors are shown here in purple. They are routed through the Body Plate, then into the Micro Plate housing. The wiring is concealed once the Micro Plate is attached to the Body Plate.

The wires are not colour coded. However should a motor turn in the wrong direction, this can be corrected in the code pin assignments.

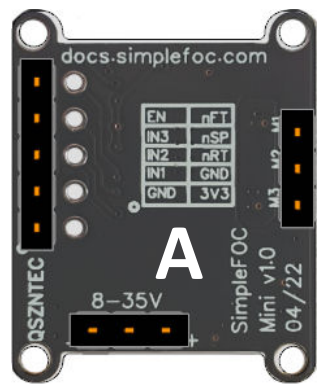
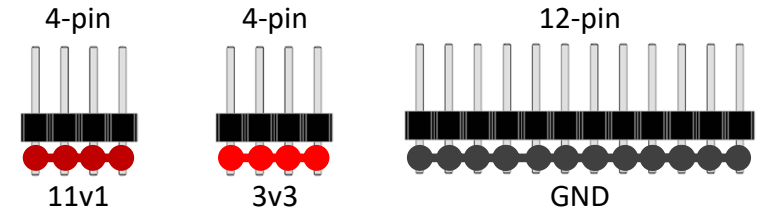
The pin strips for the common connections are prewired, shorting the pins together, before they are glued into the Micro Plate.




A



3v3, 3A buck regulator

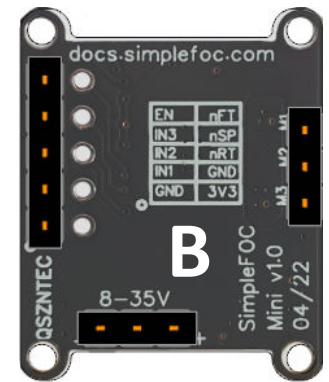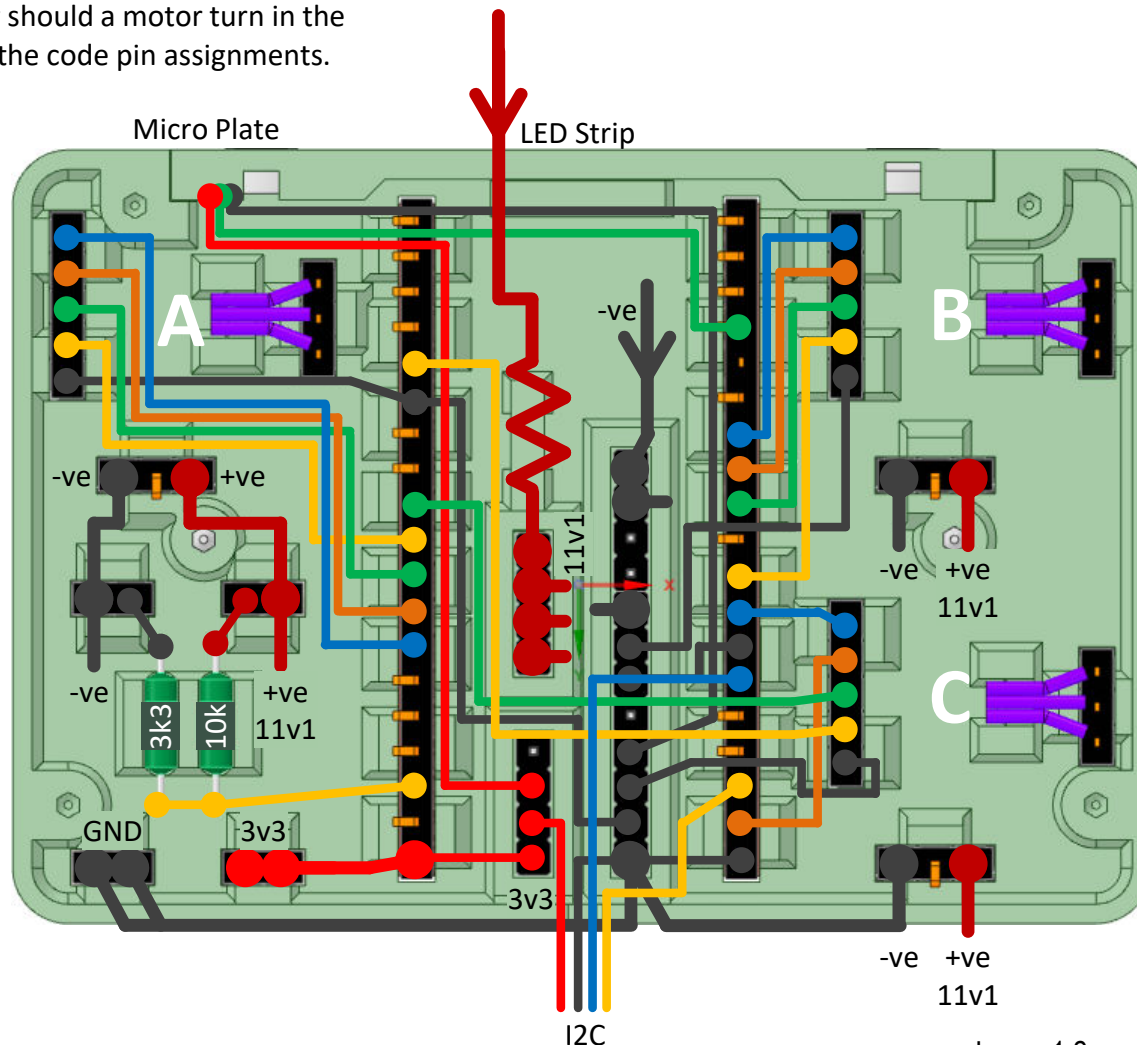

B

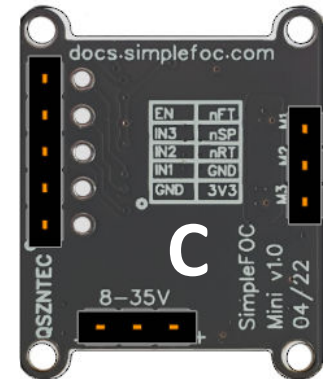

C

Micro Plate Wiring – Step 1






Start by wiring in the supply lines, and the two resistors for battery monitoring, as shown here.


Since the solder pads on the RGB LED are small and a little tricky to solder, they have been mounted in a separate strip. Which you pre-wire, prior to gluing into the main Micro Plate housing. Glue the WS2812B chips into the strip first, then wire, leaving sufficient length for connections to the ESP32 and supply lines.

Once wired into position you can temporarily insert the ESP32 micro and test the LED strip, before gluing it into the Micro Plate, using USB power fed into the micro from you PC.

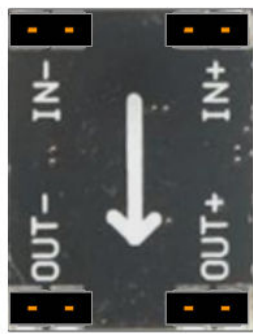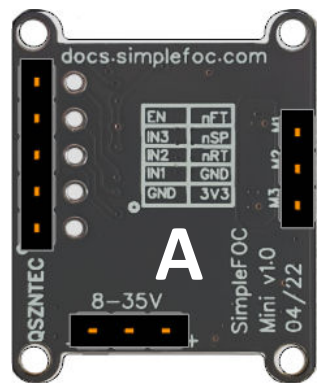
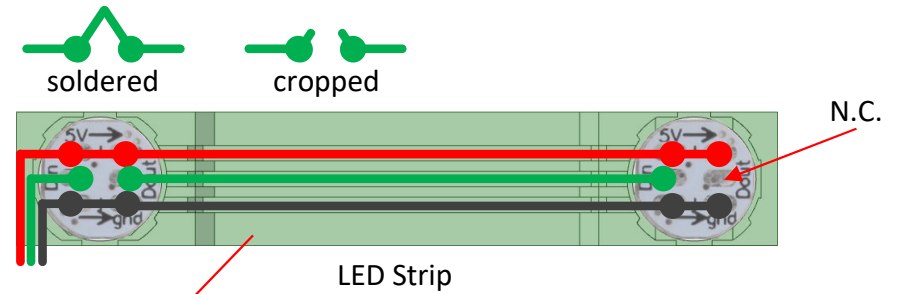
The wires running along the LED strip do not need to be insulated, as long as they are prevented from touching each other. The data wire is run in as one wire, bent up/down between the first two pads, soldered in place, and then cropped out after soldering to break the in/out data connection.



3v3, 3A buck regulator

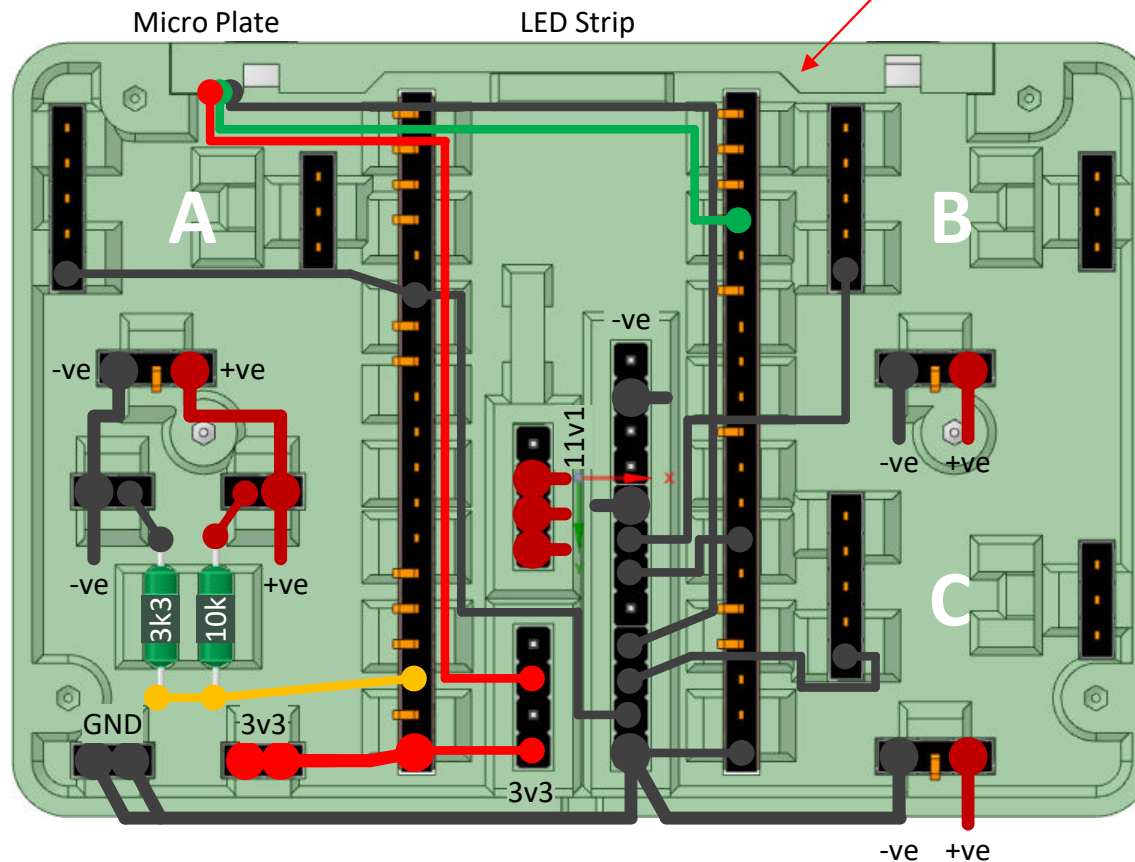

Viewed from inside the case

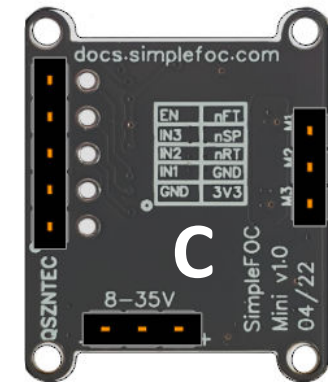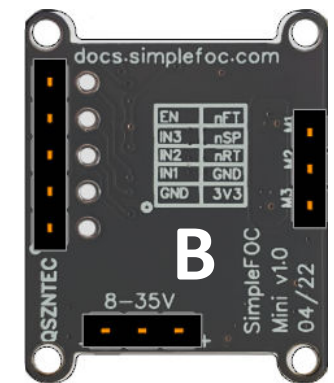

Micro Plate Wiring – Step 2


Next complete the wire wrap connections, between the ESP32 micro and the SimpleFOC mini driver boards A, B and C.

Note that the voltage regulator board is adjustable, and should be set to provide a 3v3 output, from a 12v input; either before insertion into the micro case, or with the ESP micro is not inserted.


Unused pins on the micro can be bent over, to aid the routing of wires. Once the wiring is complete, crop any excess material off the pin strips to provide more space within the micro plate case.



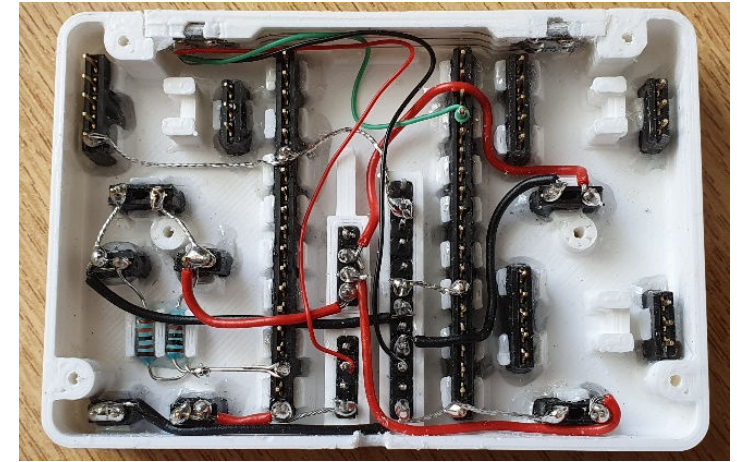The previous step should look like this as the starting point:




Battery
+ve 11.1v

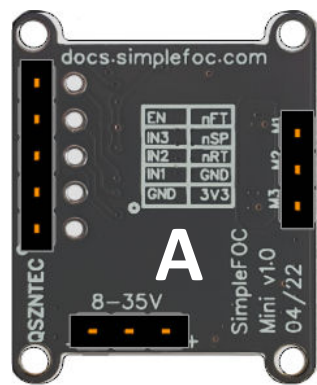

A



3v3, 3A buck
regulator

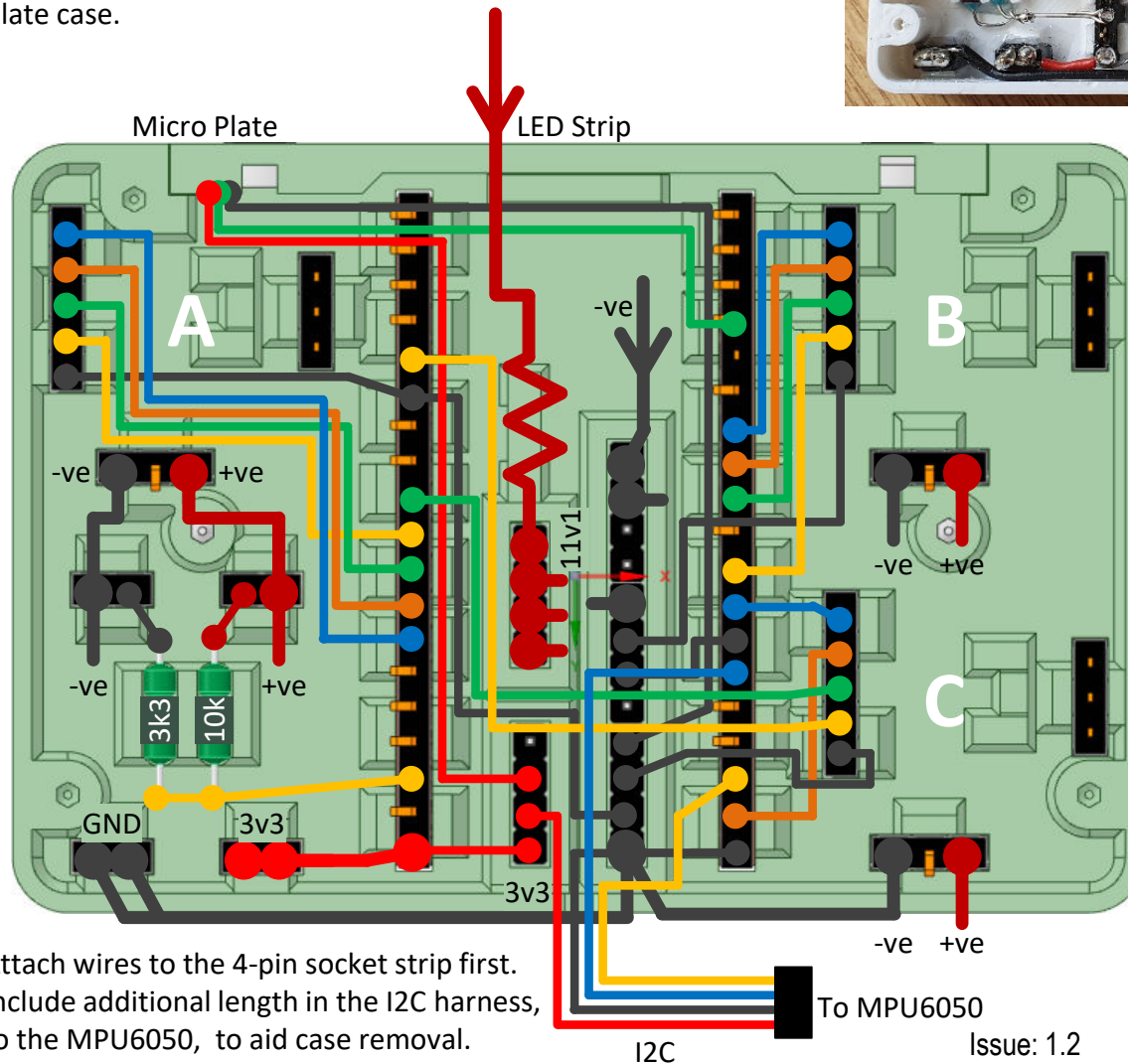

Attach wires to the 4-pin socket strip first. Include additional length in the I2C harness, to the MPU6050, to aid case removal.

I2C

To MPU6050

Issue: 1.2

Released: 08/12/2025



TechKnowTone

Micro Plate Wiring – Step 3

Then finally, wire in the three motors. If the motors happen to turn in the wrong direction, when powered up and tested, we can simply change the pin assignments in the code to correct the SimpleFOC phase orientation.




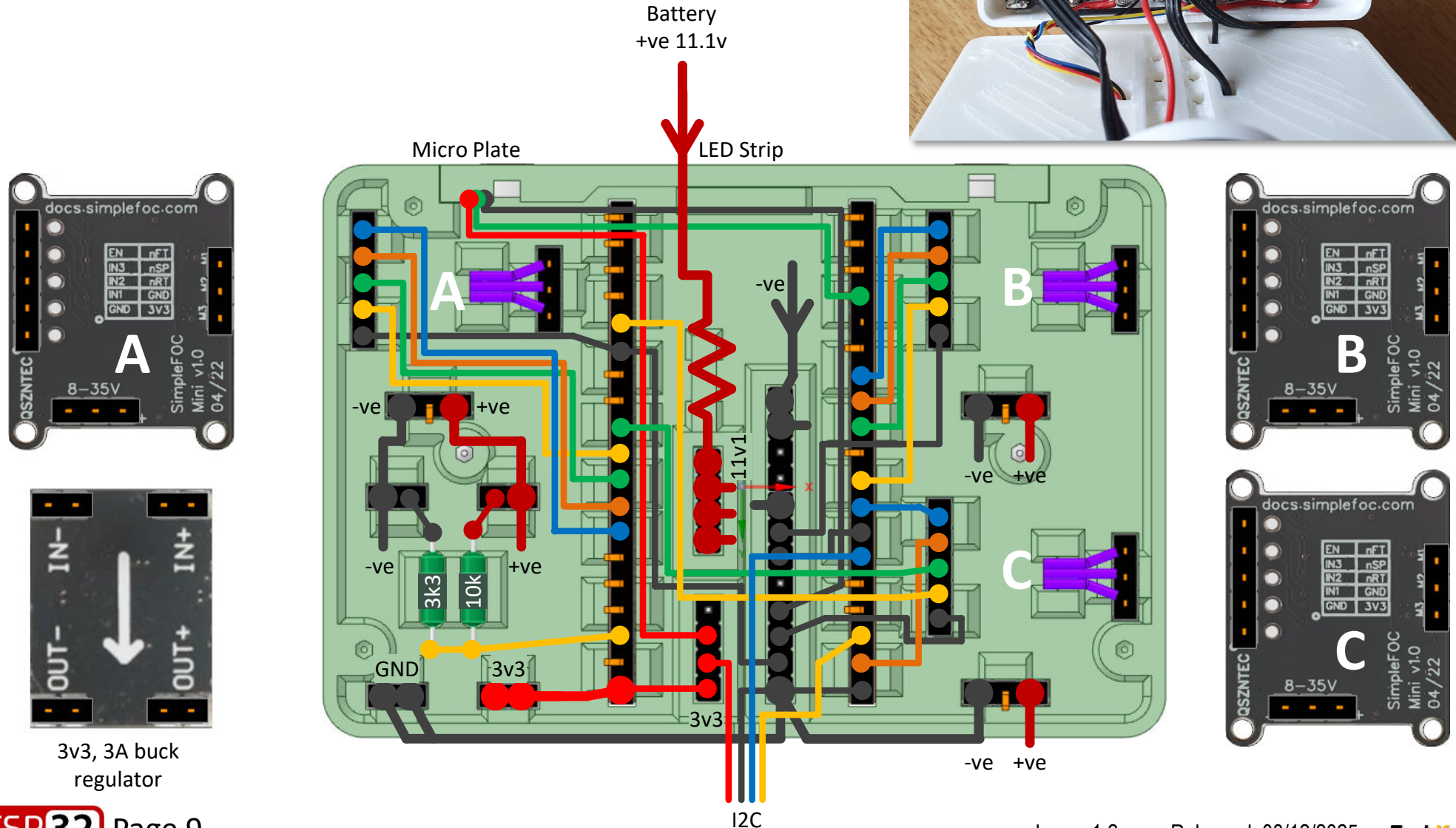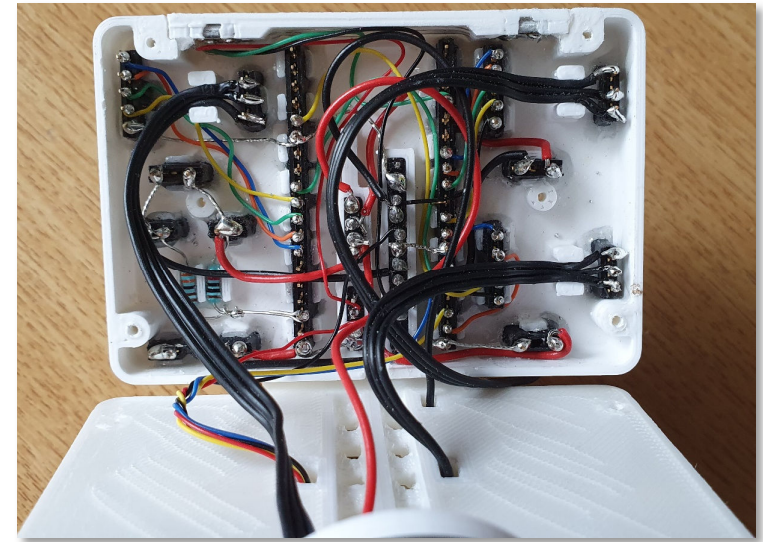The image on the right (enlarged on the next page) shows the internal wiring of my Uni-Bot micro plate housing.



3v3, 3A buck regulator






Micro Plate Wiring – Complete

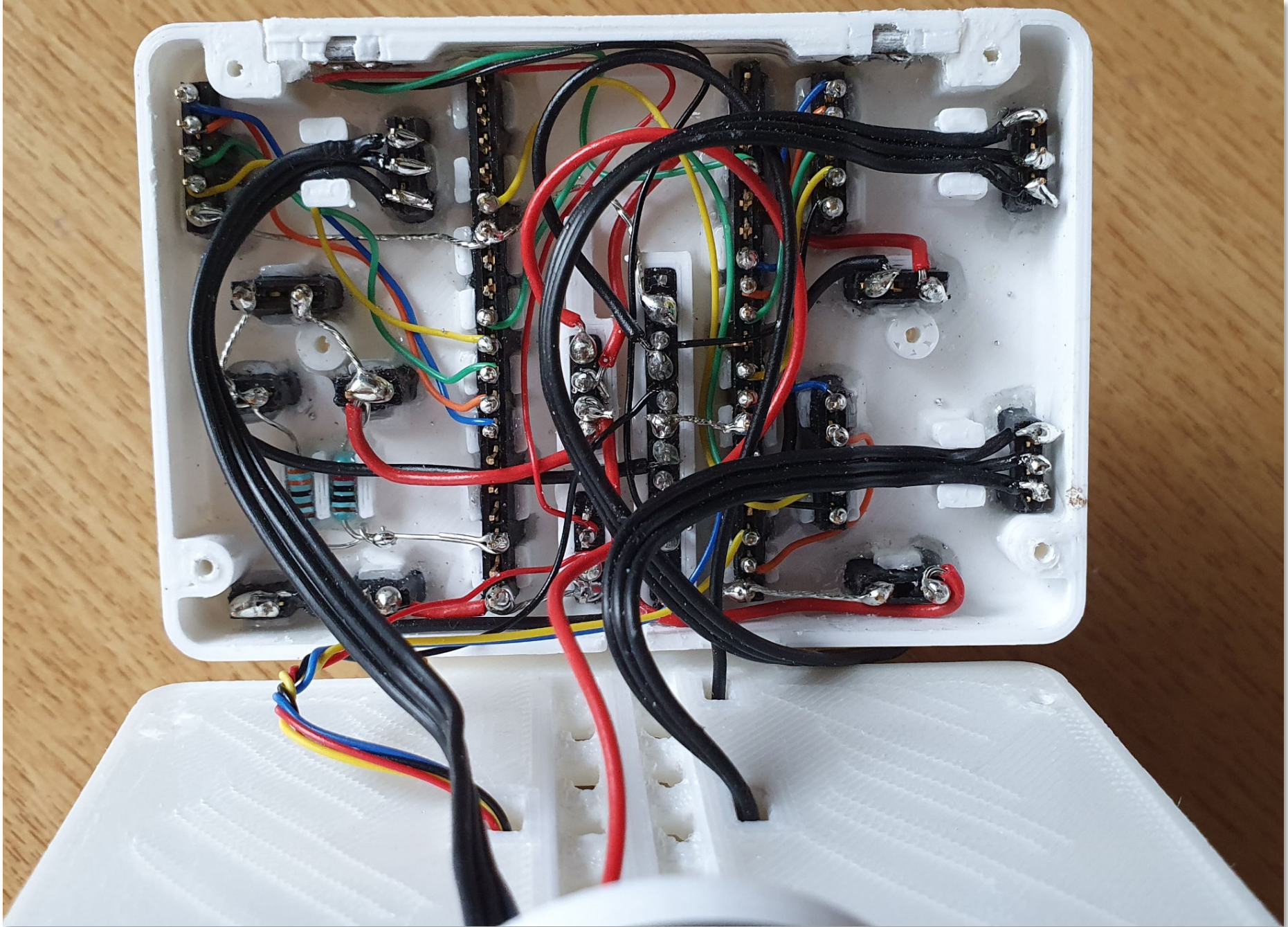

Battery Wiring

This diagram shows the wiring of the Battery Plate and the Battery Cover connections. The negative connection, of the right-hand battery, is soldered, then passed round the front of the Uni-Bot, behind the motor mount, to the positive connection of the left-hand battery.

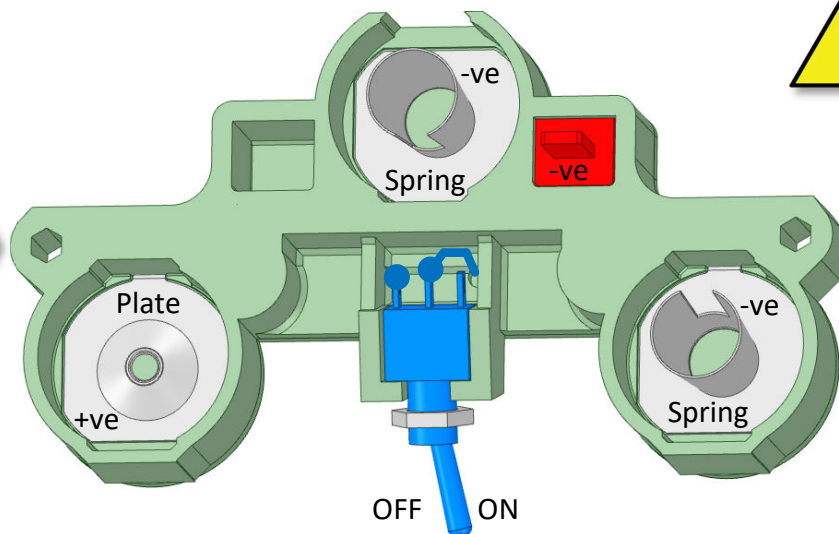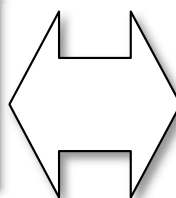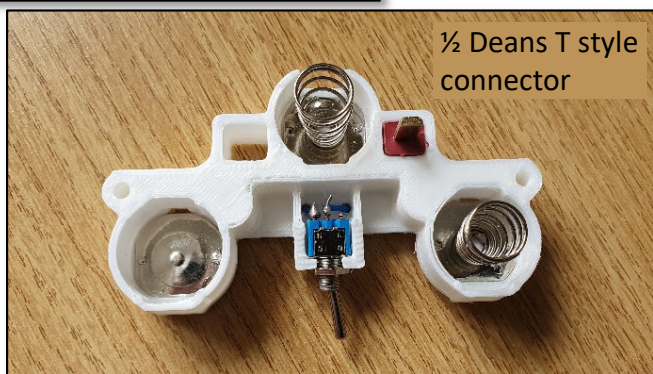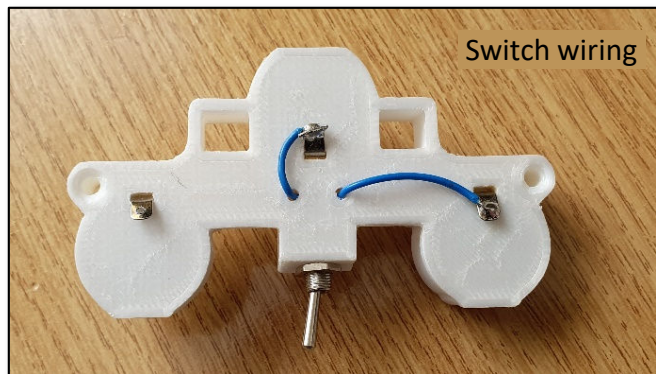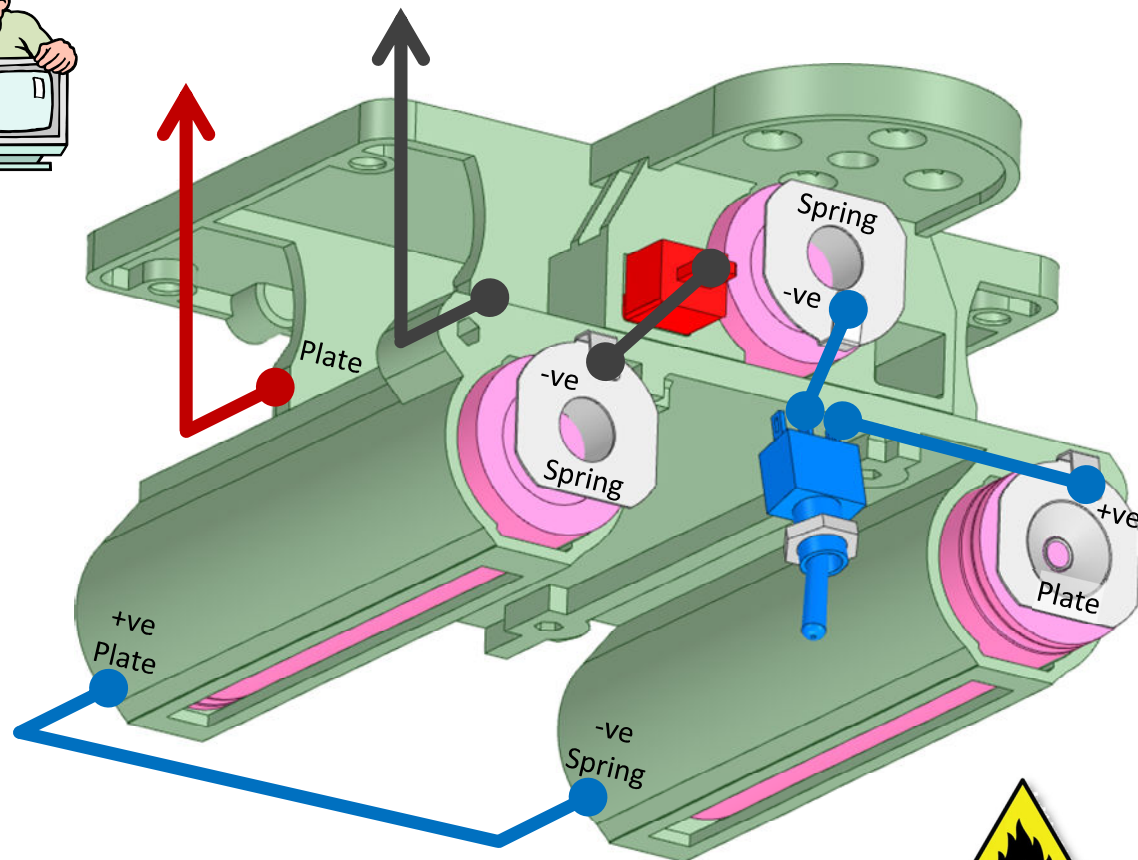The Cover Plate, Deans T battery spade connector and toggle switch are prewired before gluing the two halves of the Cover Plate together. The toggle switch connects the negative of the centre battery to the positive of the right-hand battery. The negative of the left-hand battery is wired to the spade connector.





WARNING: this design does not include any form of circuit protection, like a fuse; so considerable current can flow from the batteries if a short circuit fault occurs. There is a lot of energy stored in these batteries, so please take care, and insulate connections accordingly.

MPU6050 Wiring

The four wire I2C harness, connecting the MPU6050 sensor to the ESP32 micro, is wired to a 4-pin socket.



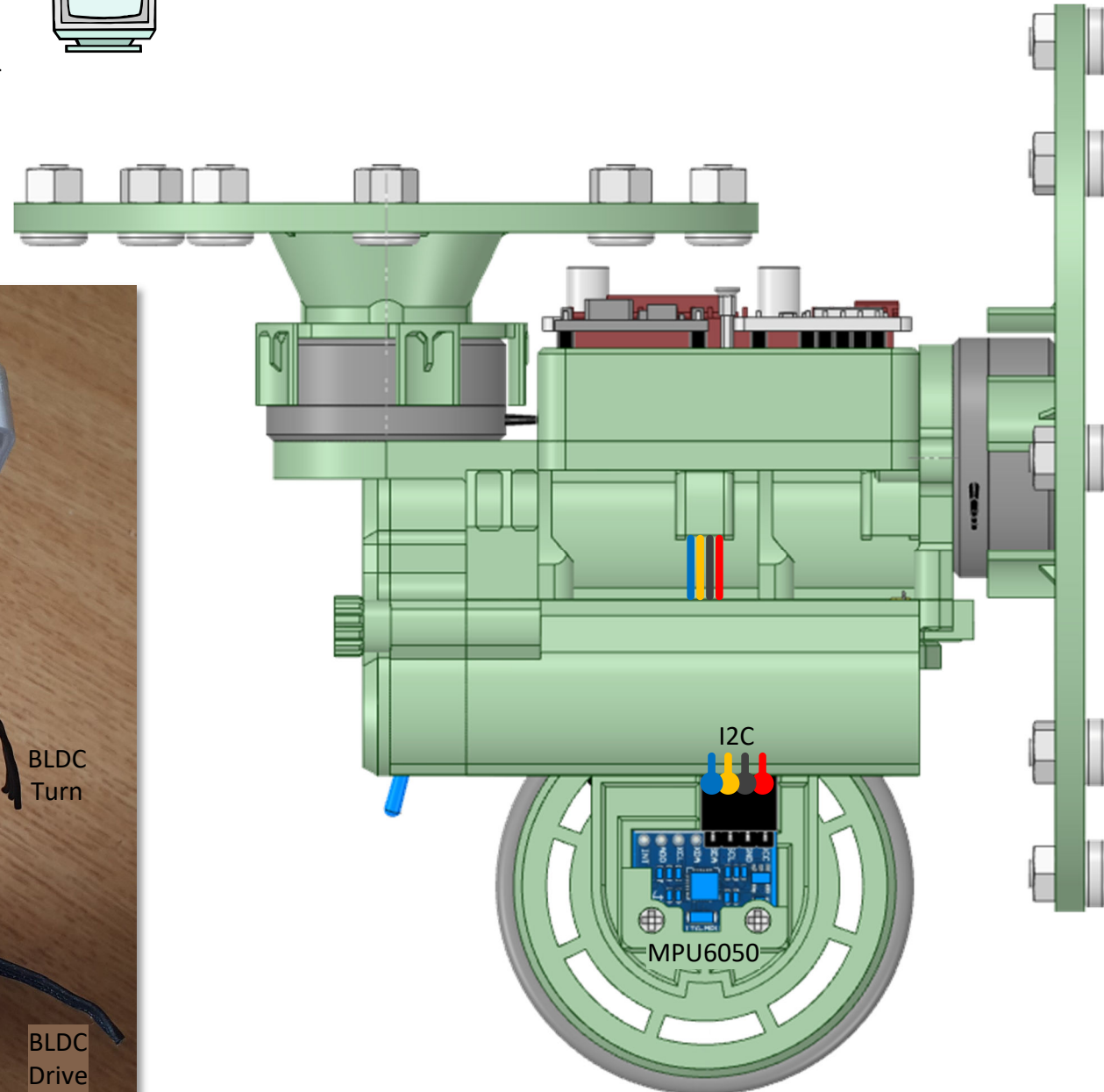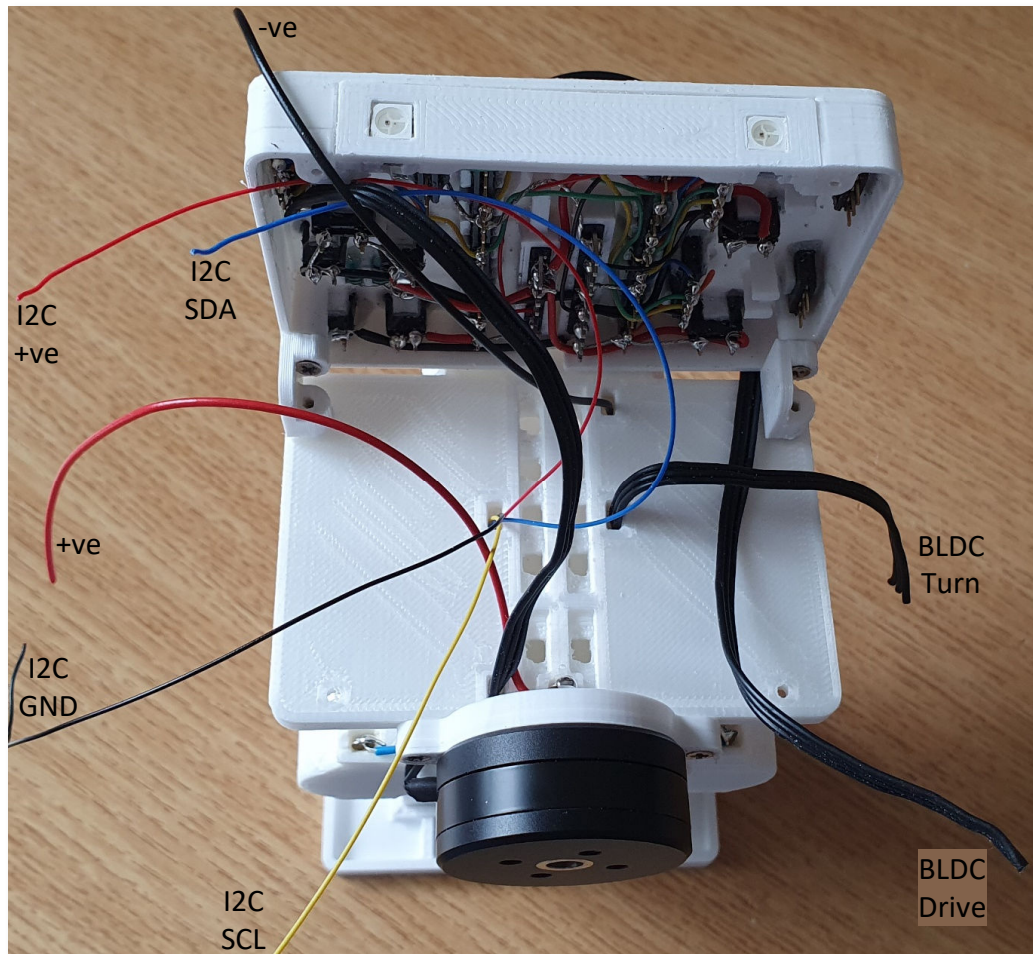I would recommend that you make this part of the harness first, prior to passing it through the body plates, to the micro housing, and then wire wrapping the connections to the ESP32 micro socket pins.



Voltage Regulator





Set up the voltage regulator independently using an external power supply and multimeter. The input voltage source should be ≥ 8 volts, and we trim the regulators output to achieve 3.3 volts. This is normally done by turning the small potentiometer on the pcb in a clock-wise direction, to reduce the output voltage.

Once the robot is wired and assembled, plug in the voltage regulator, ensuring the correct orientation, with the potentiometer and inductor towards the lower edge. Install the three batteries, and check that the output of the voltage regulator is at 3.3 volts.

Now insert the ESP32 micro, with the power off, and download the code into it. When power is re-applied, this should confirm that the RGB LED's are working. All three SimpleFOC mini drivers power LEDs should also light up.

The accuracy of the analogue to digital converter (ADC) in the ESP32 can be improved by calibrating it's measurements against a multimeter, whilst using an adjustable voltage supply. This is important for setting the correct motor PWM values, to prevent them over-heating.

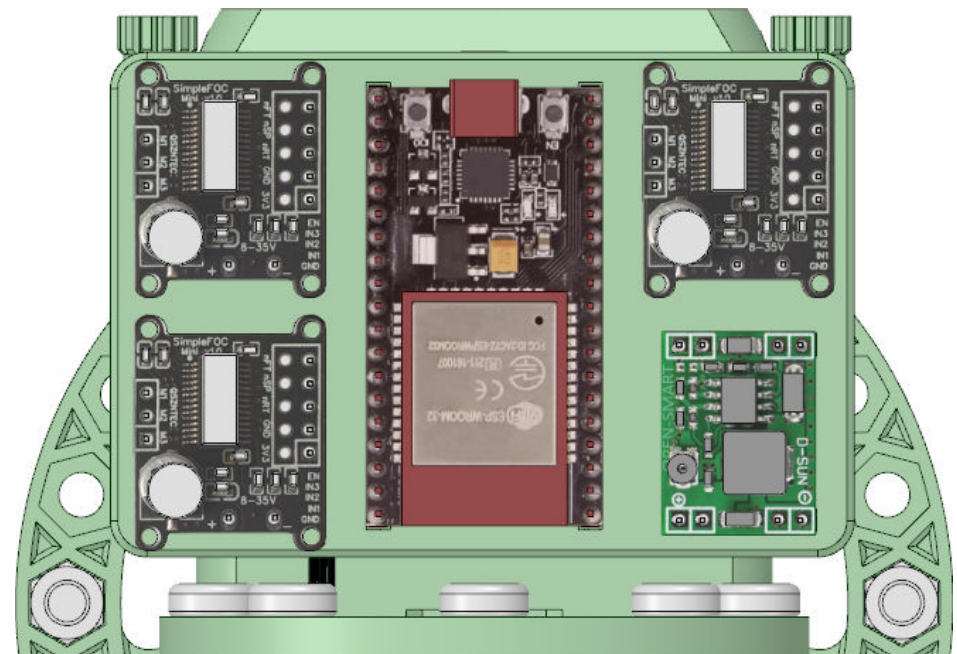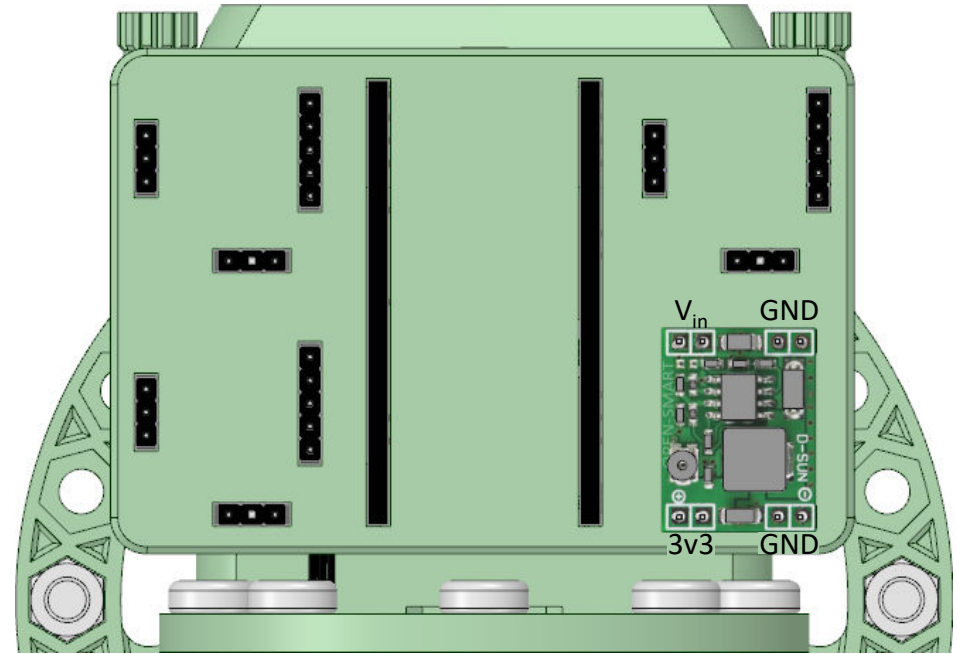I soldered a $1M\Omega$ resistor across the voltage regulators input pins, to make it easier to attach an external power supply for these measurements.



Battery Voltage Health Monitoring

See Lithium discharge curve obtained from the internet. In this analysis the lipo battery consists of three identical batteries connected in series. Assume fully charged 11.1v battery max voltage is $V_{BM} \geq 12.9v$ max
 Set battery warning point at $V_B = 10.5v$ (3 x 3.5v)
 Set battery critical point at $V_{BC} = 9.9v$ (3 x 3.3v)


The ESP32 is powered via a voltage regulator connected to the 3.3v pin. $V_{ADC} == 4095$ on 12-bit converter (4095 max).
 If we use a 10k resistor feeding A0 and a 3k3 resistor to GND, we get a conversion factor of $13.3v == 4095$, or 3.25mV/bit, or 307.9 bit/v
 Using a Multimeter I determined the following V_{ADC} values for corresponding threshold voltages:

- MAX: (100%) $V_M = 12.3v$, gave A0 = 3841 on V_{ADC} (3 x 4.1v)
- HIGH: (80%) $V_H = 11.4v$, gave A0 = 3402 on V_{ADC}
- WARNING: (20%) $V_B = 10.8v$, gives A0 = 3175 on V_{ADC}
- CRITICAL: (0%) $V_{BC} = 10.0v$, gives A0 = 2895 on V_{ADC} (3 x 3.3v+)


The code will sample the battery voltage on power-up to ensure it is sufficient, then at every 40ms interval, calculating an average (1/20) to remove noise. It also detects no battery as USB mode.

In the code I have assumed a discharge curve ranging from 12.3v (100%) to 10.0v (0%) capacity, using the overlay lines shown. The rate of discharge is monitored and used to predict the life of the battery in use.

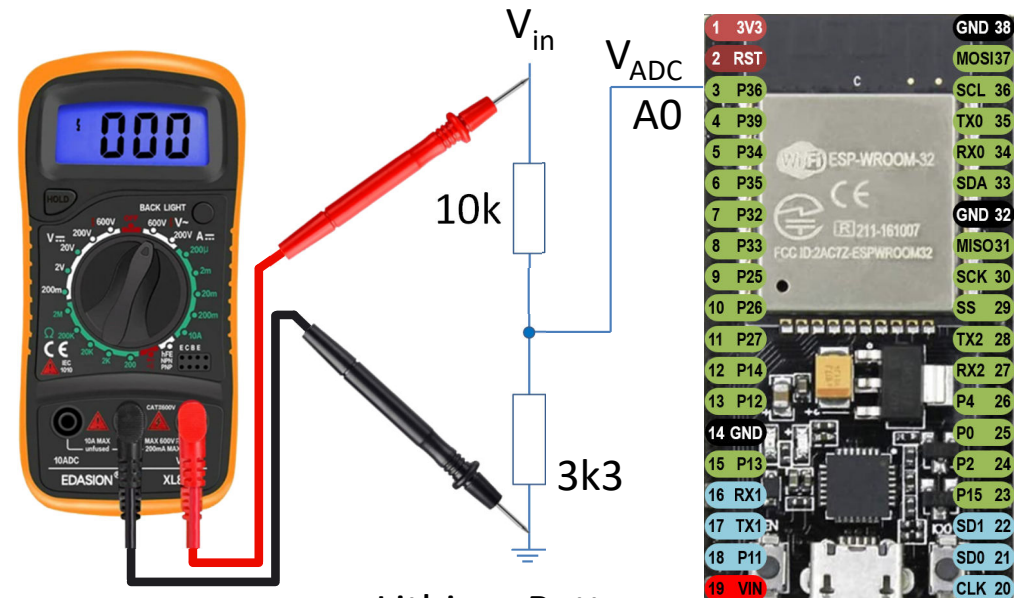
Note: If connected to USB port with internal battery switched OFF the ADC will read a value 5 volts (A0 = 1919) or less. So if the micro starts with such a low reading it knows that it is on USB power.



Lithium Battery Discharge Profile

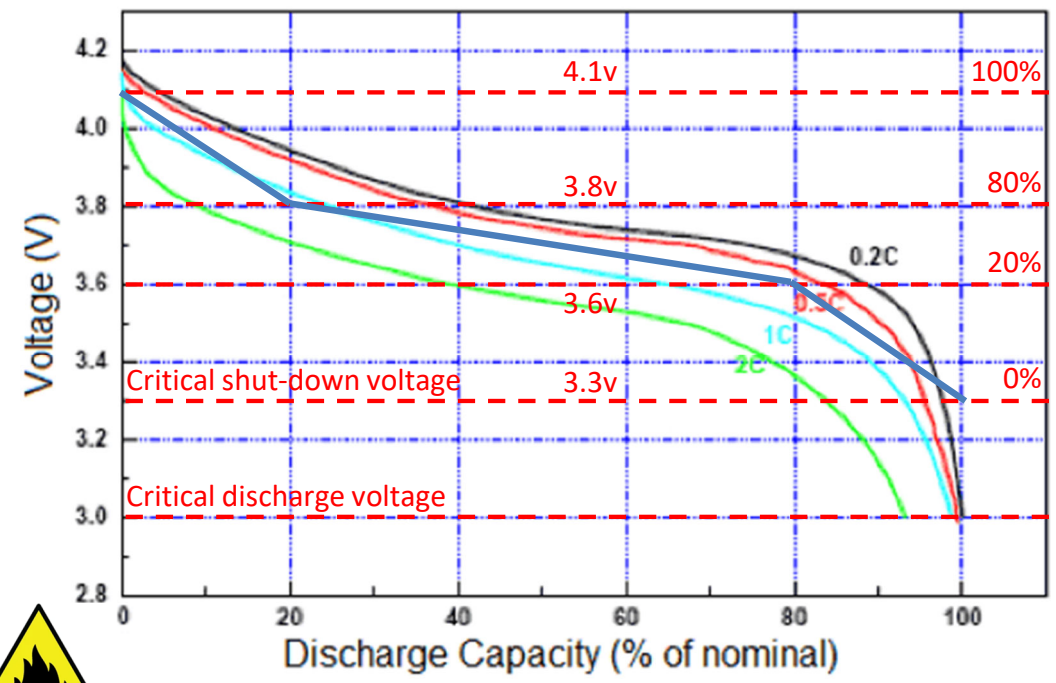


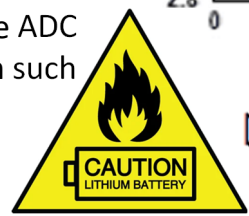Discharge: 3.0V cutoff at room temperature.




Build Images

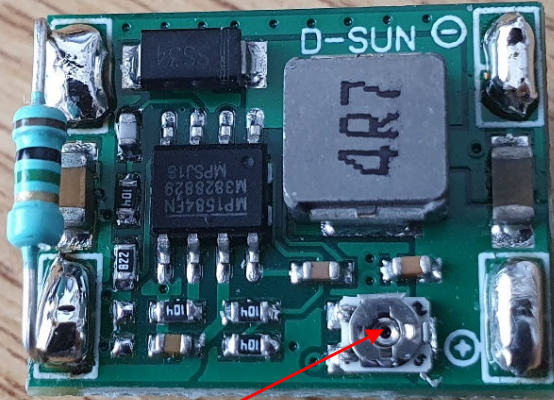01 Buck regulator with 1MΩ resistor across output



Adjust output voltage

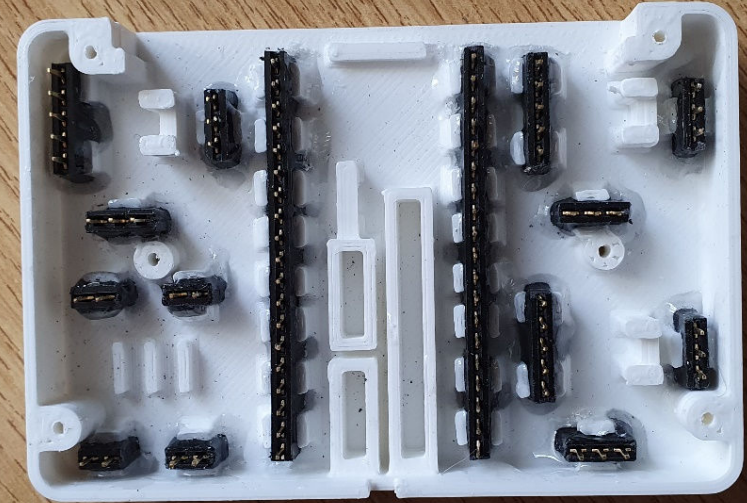02 Micro plate cover with socket strips glued in



02


03 WS2812B RGB LEDs glued into strip



Note LED orientation and direction





Apply epoxy glue sparingly and avoid solder contacts

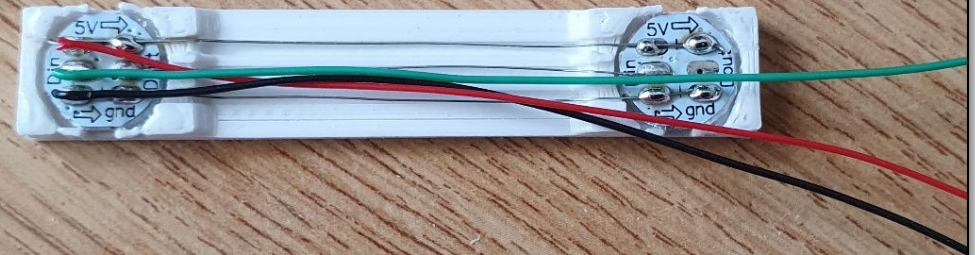04 LED strip with wires soldered in position







04

Build Images

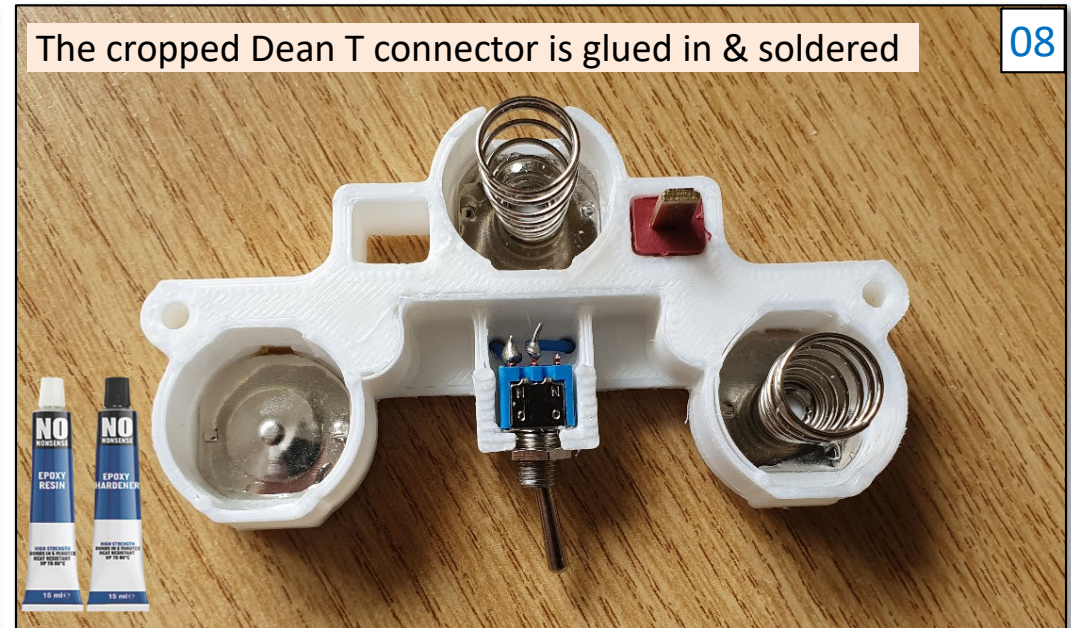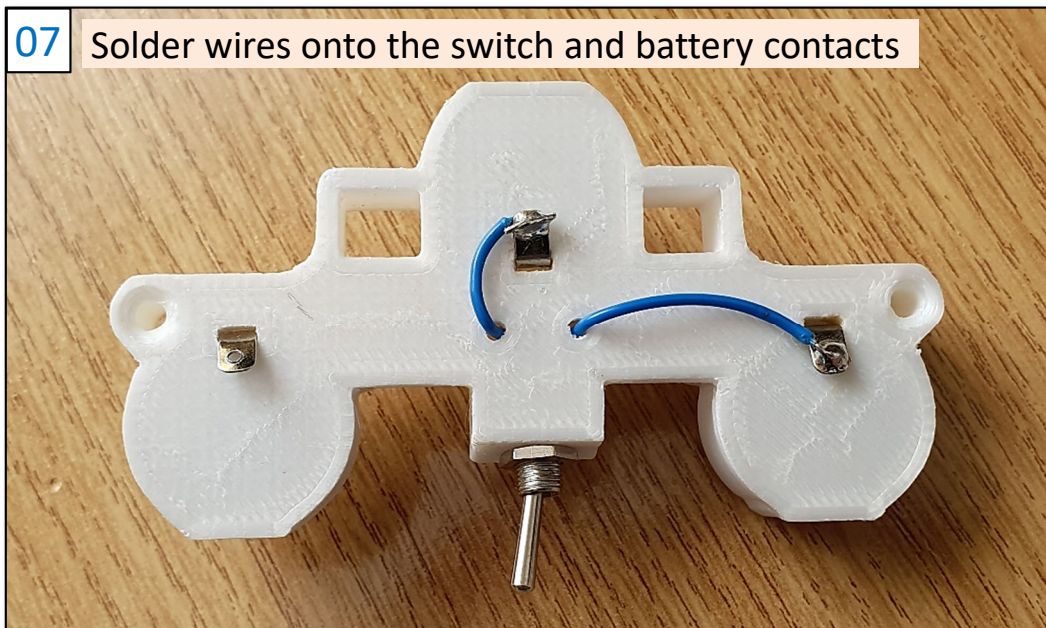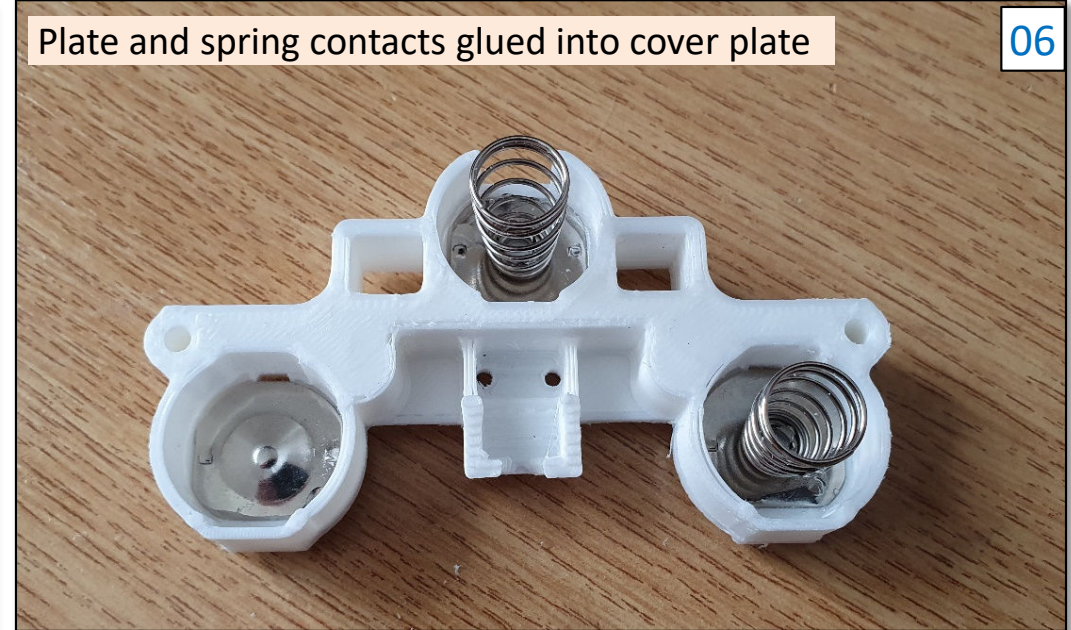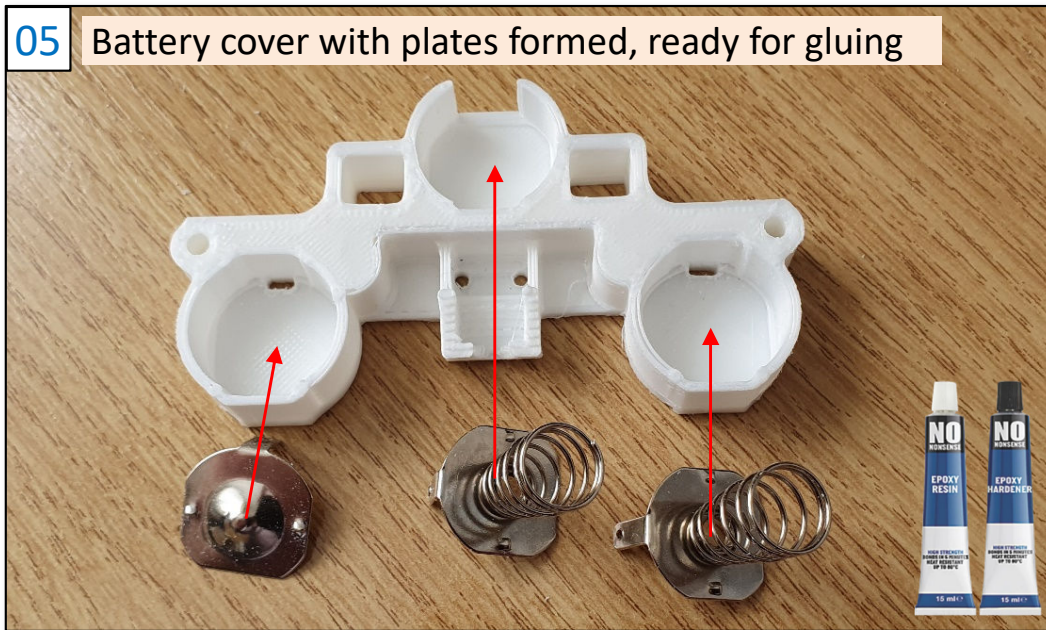


Build Images

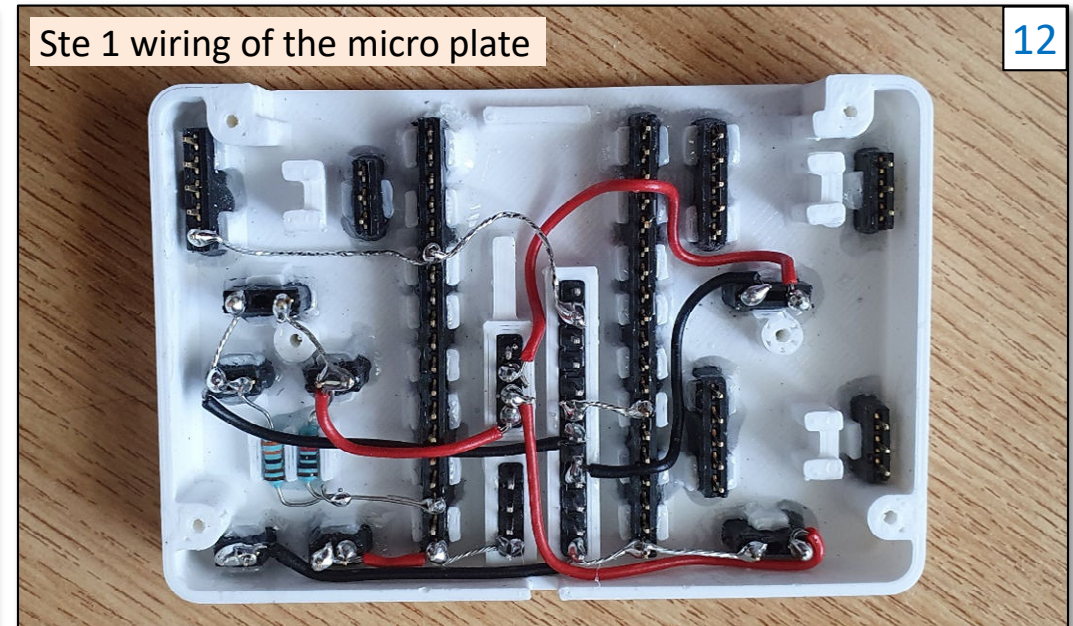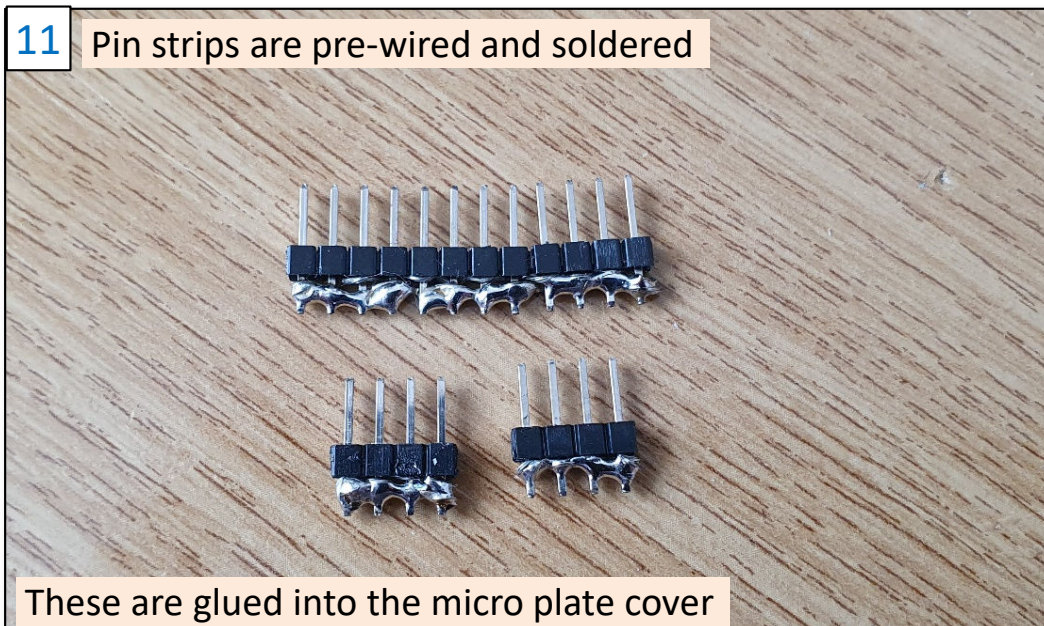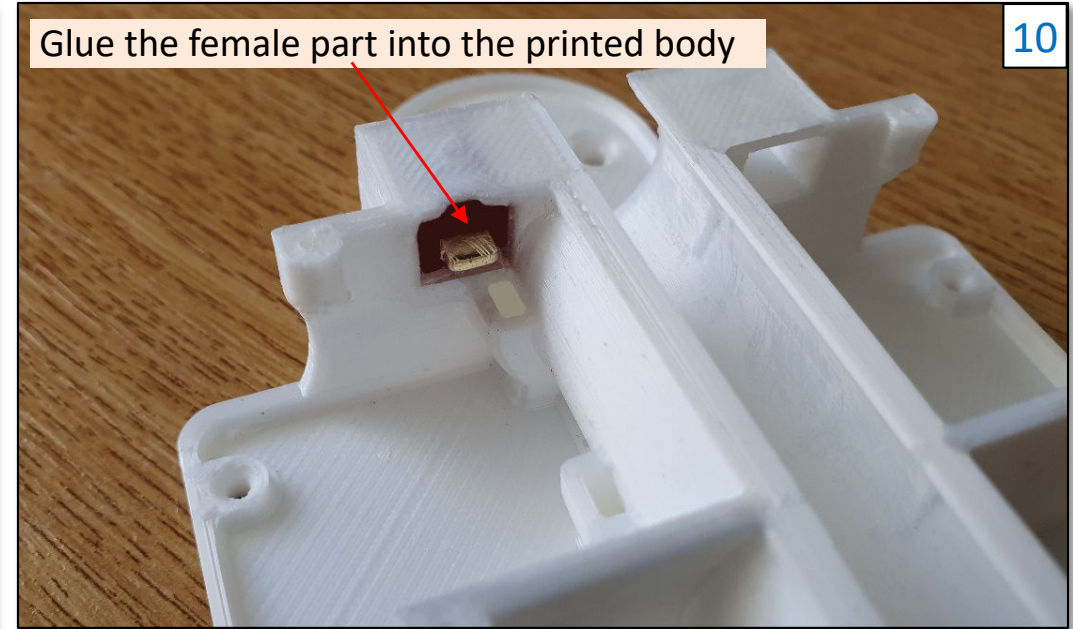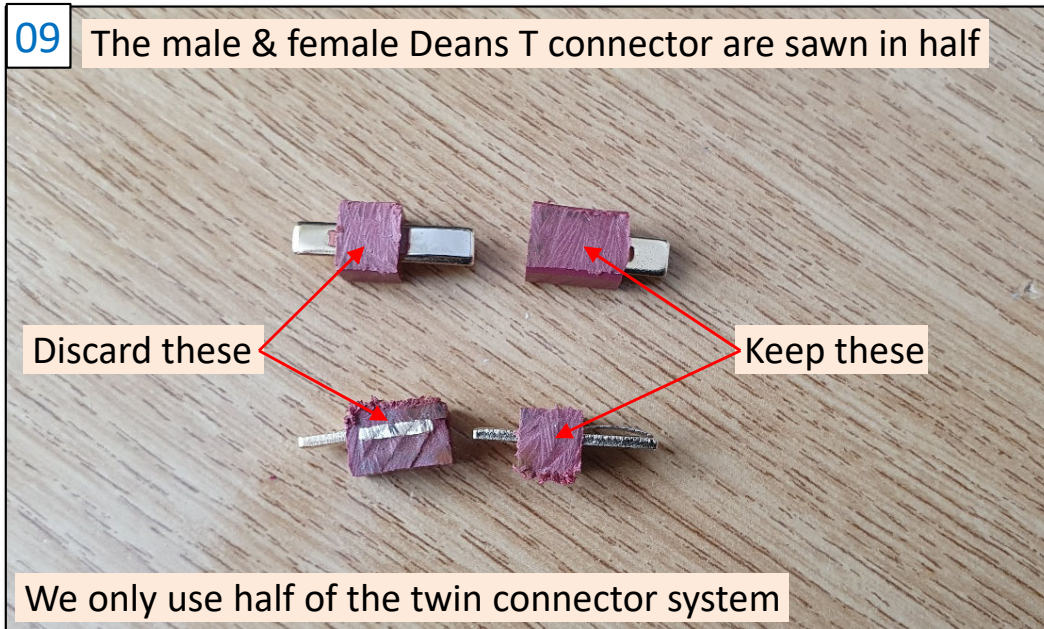


Build Images

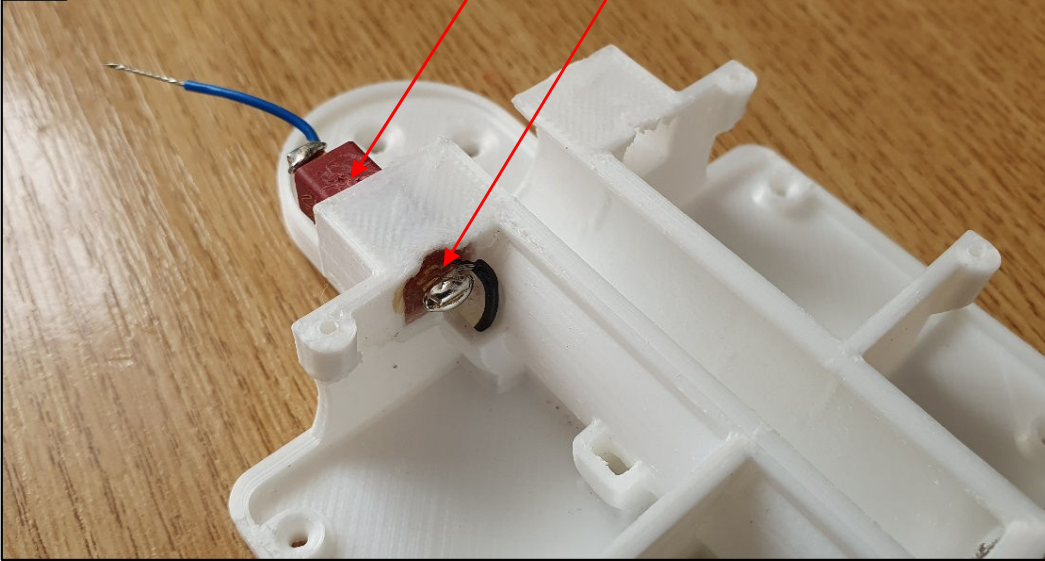
13 Solder wires onto the male & female parts



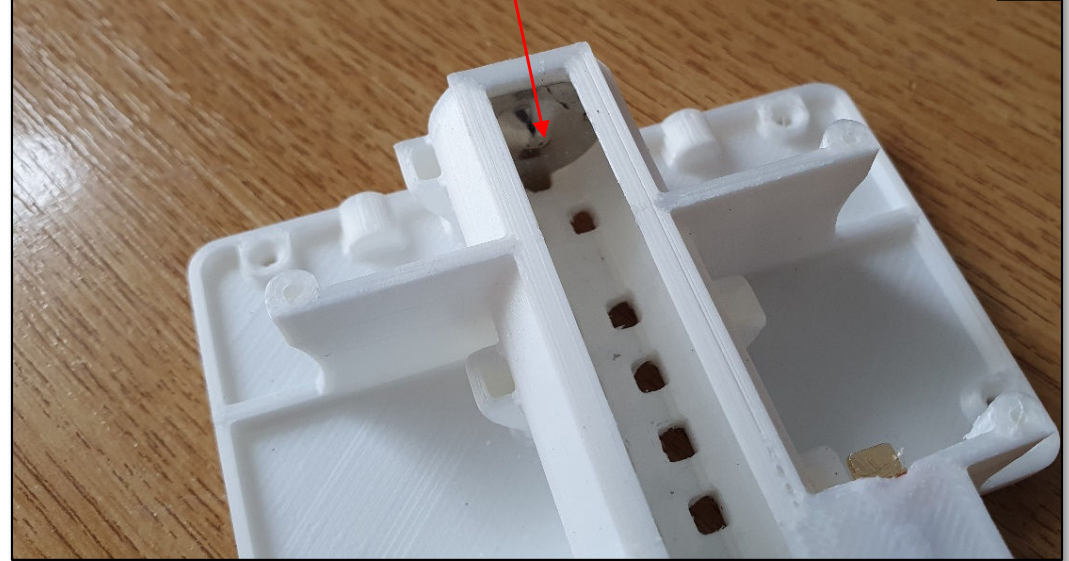
14 Glue in the +ve battery connector plate



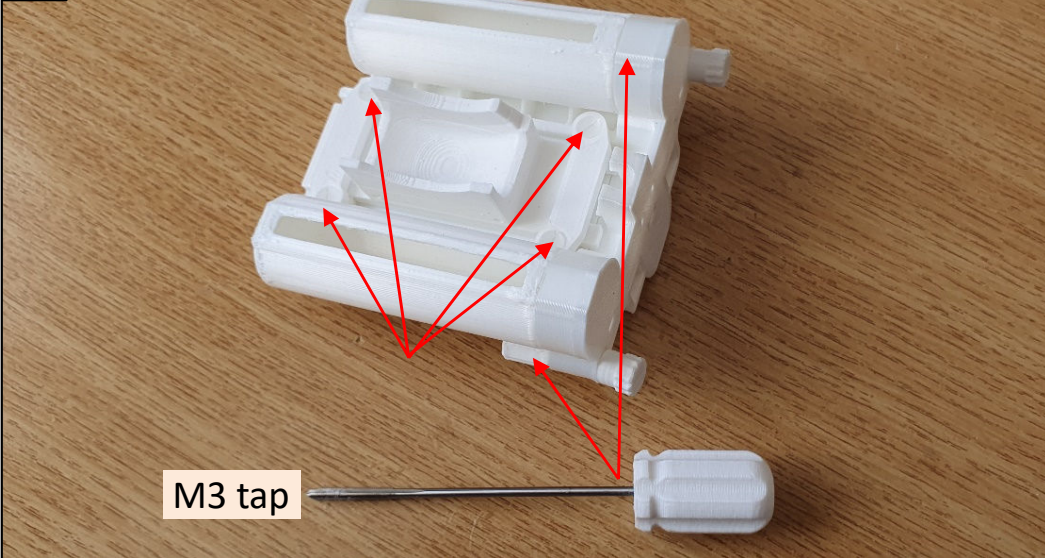15 Thread the battery plate screw holes with an M3 tap



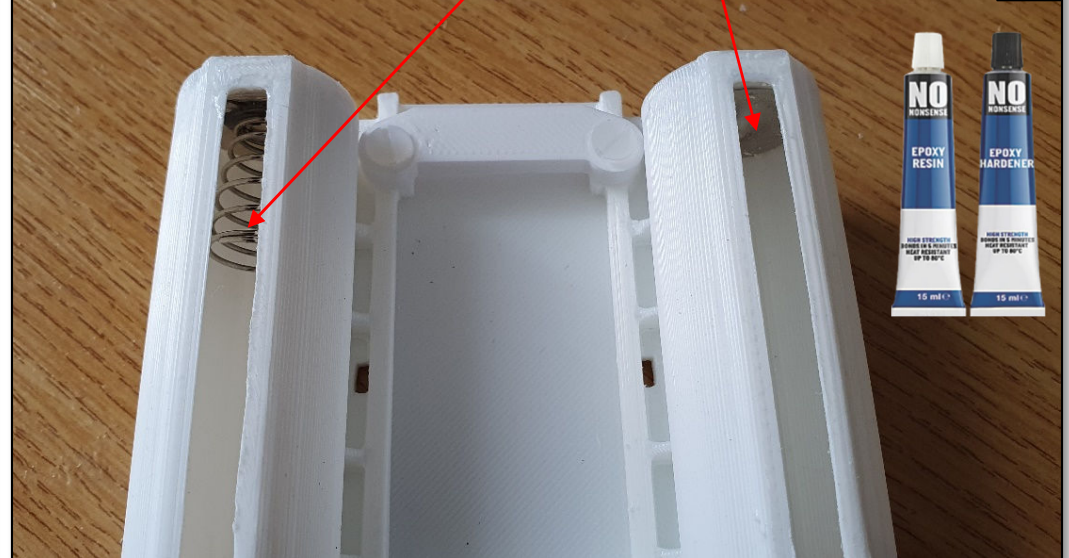16 Glue in the -ve battery spring and +ve plate



Build Images

17 The end cover for the battery cover body plate




18




Use clamps when gluing the end cover onto the body cover

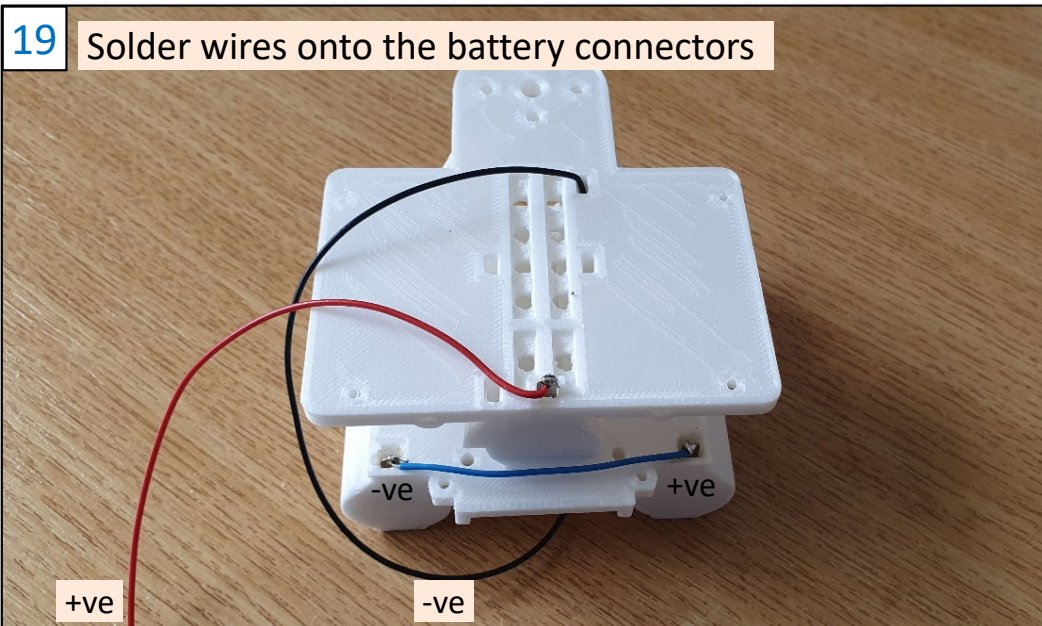19 Solder wires onto the battery connectors



20

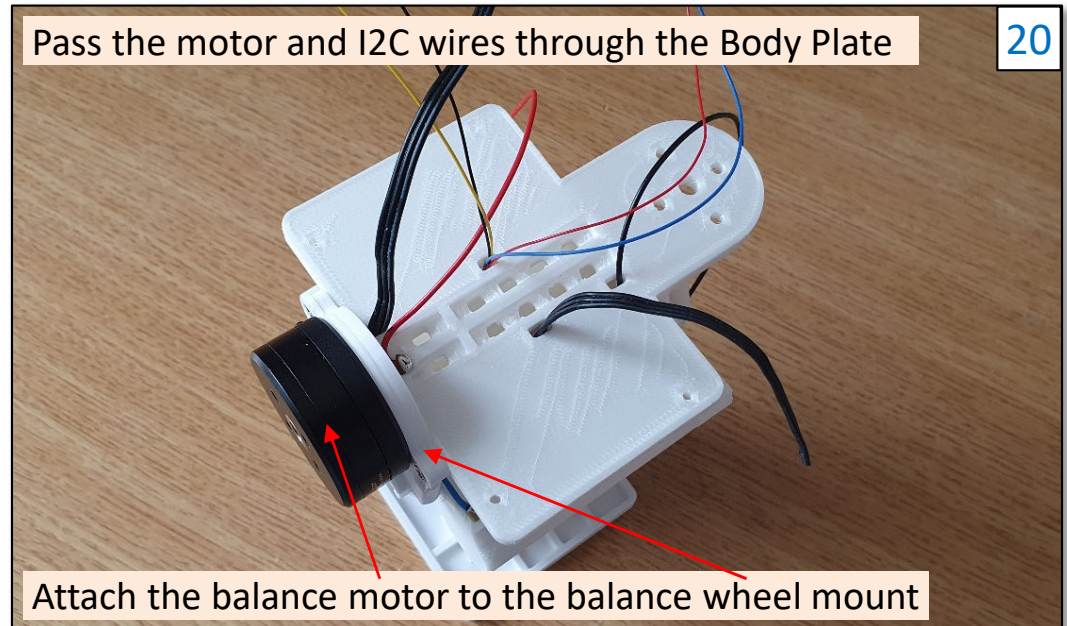
Pass the motor and I2C wires through the Body Plate



Attach the balance motor to the balance wheel mount


Build Images

21

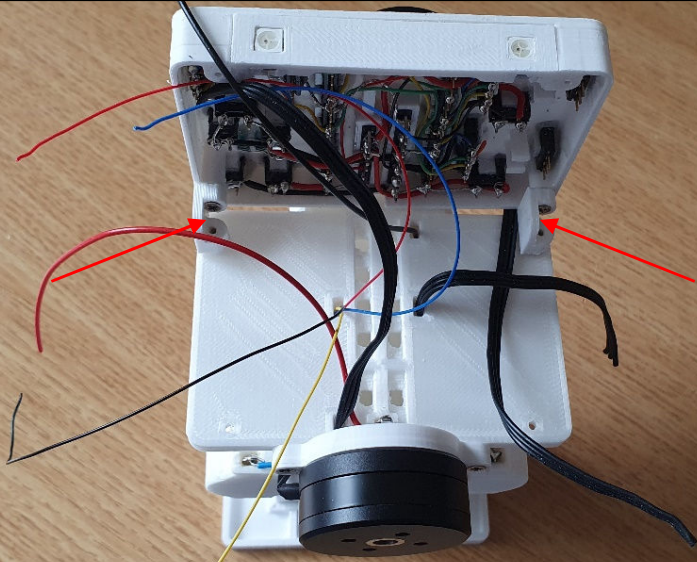


Use the small brackets to temporarily mount the micro plate

22

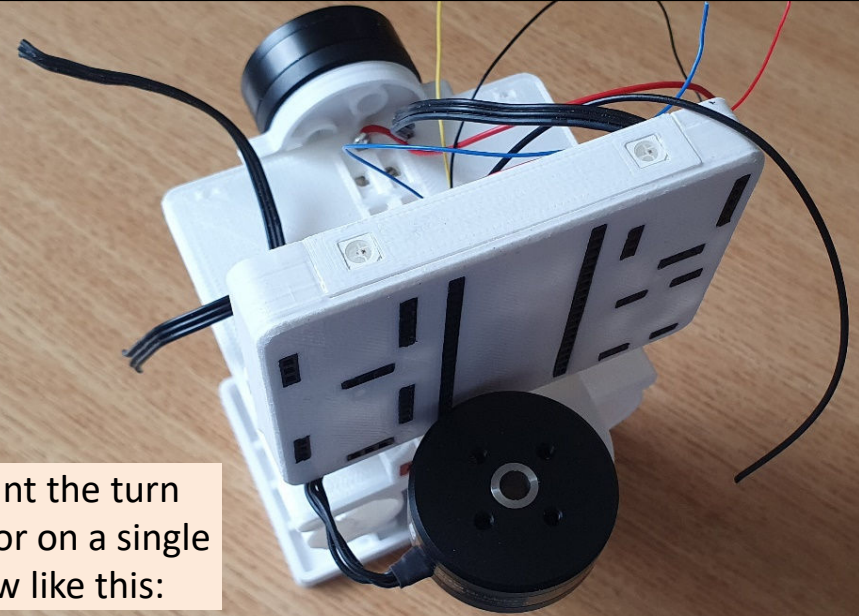

Mount the turn motor on a single screw like this:


23

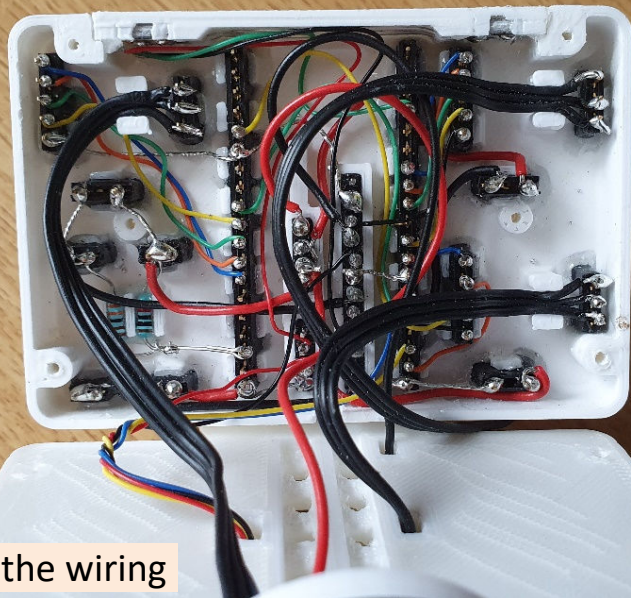

Complete the wiring


24

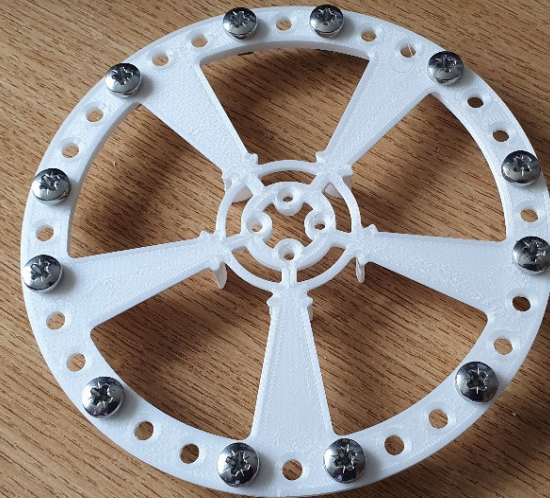Pre-load the reaction wheels with M5 nuts and bolts



I used 12 on the balance wheel and 8 on the turn wheel

Finally...

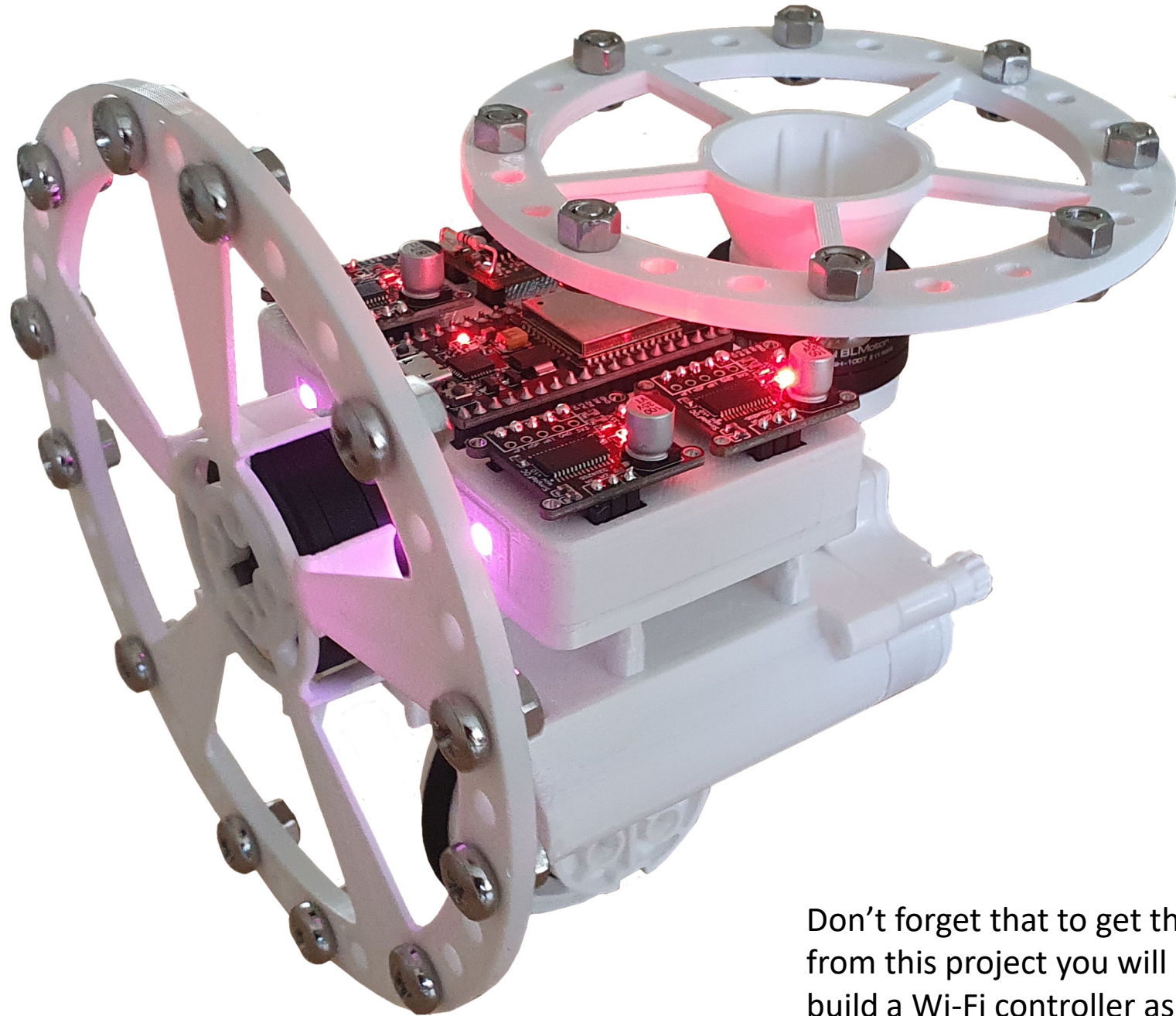

Don't forget that to get the most from this project you will need to build a Wi-Fi controller as well.

